

Advanced Digital Logic Design – EECS 303

<http://ziyang.eecs.northwestern.edu/eecs303/>

Teacher: Robert Dick
Office: L477 Tech
Email: dickrp@northwestern.edu
Phone: 847-467-2298



NORTHWESTERN
UNIVERSITY

Combinational testing
Sequential testing

Yield
Fault models
Combinational test generation

Introduction to testing

- After fabrication, some circuits don't work correctly
- Determining which circuits contain faults requires testing
- Testing some types of circuits is easy, testing others is difficult
 - One can use automation to help solve this problem

3

Robert Dick

Advanced Digital Logic Design

Combinational testing
Sequential testing

Yield
Fault models
Combinational test generation

Yield

- Yield, y , is the fraction of fault-free products
- Test fault coverage, c , is the fraction of faults that the set of applied tests detects
 - Low-yield is expensive because fabrication capacity is wasted
- Defect level, d , is the fraction of parts containing undetected faults
 - $d = 1 - y^{1-c}$
 - A high defect level is extremely expensive because it means circuits make their way into products, or worse, to consumers, before faults are discovered

6

Robert Dick

Advanced Digital Logic Design

Combinational testing
Sequential testing

Yield
Fault models
Combinational test generation

Faults and failures

- A *fault* is a physical defect in a circuit
- A *failure* is the deviation of a circuit from its specified behavior
- Faults can cause failures but they don't always cause failures

9

Robert Dick

Advanced Digital Logic Design

Combinational testing
Sequential testing

Yield
Fault models
Combinational test generation

Structural testing

- Use information about the specific CUT
 - Types of faults that are likely to occur
 - Structure of circuit

11

Robert Dick

Advanced Digital Logic Design

Combinational testing
Sequential testing

Yield
Fault models
Combinational test generation

Introduction to testing

- Determining the best way to test large circuits requires automation
- Building large circuits that are easy to test also requires automation
- Testing it spans all design, from system to physical level
- Today, I'll introduce some classical ideas at the logic level

4

Robert Dick


Advanced Digital Logic Design

Combinational testing
Sequential testing

Yield
Fault models
Combinational test generation

Defect level

 - Example acceptable defect level: ~ 0.0002
- Either yield must be very high or fault coverage must be very high



7

Robert Dick

Advanced Digital Logic Design

Combinational testing
Sequential testing

Yield
Fault models
Combinational test generation


Functional testing

- No assumptions about types of fault
- No assumptions about structure or properties of Circuit Under Test (CUT)
- The CUT is a black box that is checked to determine whether it responds to all (or most) input (sequences) as specified
- However, ignoring structural information makes testing unnecessarily slow

10

Robert Dick

Advanced Digital Logic Design

 

Consider a NAND3 gate

Inputs			fault free	z						
A	B	C		0	1	0	1	0	1	
0	0	0	1	1	1	1	1	1	0	1
0	0	1	1	1	1	1	1	1	0	1
0	1	0	1	1	1	1	1	1	0	1
0	1	1	1	1	0	1	1	1	0	1
1	0	0	1	1	1	1	1	1	0	1
1	0	1	1	1	1	0	1	1	0	1
1	1	0	1	1	1	1	1	0	0	1
1	1	1	0	1	0	1	0	1	0	1

Too expensive to use 2^n inputs ($2^3 = 8$ in this case)
Unate covering again

- The function of the circuit is identical in the presence of either fault
- E.g., any input of a NAND gate being s-a-0 or the output being s-a-1 \rightarrow output of 1
- In general, identifying equivalent faults, or *fault collapsing* is difficult
- However, can use knowledge about gates, and connectivities, to find most equivalent faults

- $\sim 2/3$ CMOS faults are not stuck-at faults
 - Luckily, stuck-at fault tests often detect them
- More advanced faults models
 - Allow higher theoretical coverage
 - Are more complicated
- In this lecture, we only have time to cover stuck-at-faults

- One of the simplest and most common fault models
 - S-a-0: Stuck-at 0
 - S-a-1: Stuck-at 1
- Relies on digital reinforcement
 - $0.8 \cdot V_{DD}$ is $1 \cdot V_{DD}$ one logic stage later
 - S-a-0.8 \approx s-a-1
- For two-level logic, exhaustive test set for single stuck-at faults will detect all multiple stuck-at faults, too
 - Doesn't hold for multi-level logic


- A test of all possible inputs for a NAND n gate will require 2^n tests
- Applying all possible tests (or sequences of tests) for complex circuits isn't practical
- However, for all NAND n gates, all single stuck-at faults (and implicitly multiple stuck-at faults) can be tested using only $n + 1$ tests

Consider a NAND3 gate

Inputs			fault free	z						
A	B	C		0	1	0	1	0	1	
0	0	0	1	1	1	1	1	1	0	1
0	0	1	1	1	1	1	1	1	0	1
0	1	0	1	1	1	1	1	1	0	1
0	1	1	1	1	0	1	1	1	0	1
1	0	0	1	1	1	1	1	1	0	1
1	0	1	1	1	1	0	1	1	0	1
1	1	0	1	1	1	1	1	1	0	1
1	1	1	0	1	0	1	0	1	0	1

Equivalent faults


 
- Can use algorithms to automatically generate a test for a specific fault
- Problem: Identify some test, t , such that the output of the circuit will deviate from its specified value if a particular fault, f , is present
- Excitation: Need to propagate a value to stuck-at fault that is contrary to the fault value
- Sensitization: Need to propagate the faulty value to an output of the circuit



- Can automatically determine test for a particular fault
- Boolean difference
 - Generally considered too slow for use on large circuits
 - Easy to understand
- Excitation/sensitization based methods (*D*-algorithm)

- If the resulting function is 0, the fault can not be identified
- If the resulting function is 1, the fault can be identified
 - Use a test that satisfies (sets to 1) the function

  - We have seen that, in order to test for a particular fault, we must
 - Excite the fault
 - Sensitize a path from the fault to the output
- The *D*-algorithm is an automated method of finding a test that excites a fault and sensitizes a path to the circuit output
- J.P. Roth, IBM, 1966



In the presence of the fault, function is \bar{i}_3
XOR faulty and specified functions

	00	01	11	10
0	1	0	0	1
1	1	0	0	0

	00	01	11	10
0	0	0	0	0
1	0	0	0	1

	00	01	11	10
0	1	0	0	1
1	1	0	0	1

- α/β
 - α is the fault-free value
 - β is the value in the presence of the fault
- $0/0 = 0$
- $1/1 = 1$
- $1/0 = \mathcal{D}$
- $0/1 = \overline{\mathcal{D}}$
- $X/X = X$

gate	detection input		\mathcal{D} -cube of failure			
	a	b	z	a	b	z
AND	1	1	s-a-0	1	1	\mathcal{D}
	0	X	s-a-1	0	X	$\overline{\mathcal{D}}$
	X	0	s-a-1	X	0	$\overline{\mathcal{D}}$
NAND	1	1	s-a-1	1	1	$\overline{\mathcal{D}}$
	0	X	s-a-0	0	X	\mathcal{D}
	X	0	s-a-0	X	0	\mathcal{D}


input		AND	NAND
a	b	z	z
1	\mathcal{D}	\mathcal{D}	$\overline{\mathcal{D}}$
1	$\overline{\mathcal{D}}$	$\overline{\mathcal{D}}$	\mathcal{D}
\mathcal{D}	1	\mathcal{D}	$\overline{\mathcal{D}}$
$\overline{\mathcal{D}}$	1	$\overline{\mathcal{D}}$	\mathcal{D}
\mathcal{D}	\mathcal{D}	\mathcal{D}	$\overline{\mathcal{D}}$
$\overline{\mathcal{D}}$	$\overline{\mathcal{D}}$	$\overline{\mathcal{D}}$	\mathcal{D}

- Initially, all the lines in the circuit are X (DON'T CARE)
 - Left blank in example
- A gate with an input of \mathcal{D} or $\overline{\mathcal{D}}$ and an output of X belongs to the *frontier*
- An element whose assigned inputs do not imply the output is *unjustified*
- We want to drive the frontier to a circuit output (sensitize)...
- ...and justify the gate inputs (excite)

Select a \mathcal{D} -cube of failure to excite the fault
while frontier has not yet reached an output **do**
 Perform the implications of the most recent assignment
if the frontier is empty **then**
 BACKTRACK
end if
 Choose a signal, s , s.t. s can't reached from the fault
 Assign s to a value in order to propagate the fault forward
end while
for each unjustified line, l **do**
 if l can be justified **then**
 Justify l
 else
 BACKTRACK
 end if
end for
 A test has been found


gate	detection input		\mathcal{D} -cube of failure			
	a	b	z	a	b	z
OR	0	0	s-a-1	0	0	$\overline{\mathcal{D}}$
	1	X	s-a-0	1	X	\mathcal{D}
	X	1	s-a-0	X	1	\mathcal{D}
NOR	0	0	s-a-0	0	0	\mathcal{D}
	1	X	s-a-1	1	X	$\overline{\mathcal{D}}$
	X	1	s-a-1	X	1	$\overline{\mathcal{D}}$

input		OR	NOR
a	b	z	z
0	\mathcal{D}	\mathcal{D}	$\overline{\mathcal{D}}$
0	$\overline{\mathcal{D}}$	$\overline{\mathcal{D}}$	\mathcal{D}
\mathcal{D}	0	\mathcal{D}	$\overline{\mathcal{D}}$
$\overline{\mathcal{D}}$	0	$\overline{\mathcal{D}}$	\mathcal{D}
\mathcal{D}	\mathcal{D}	\mathcal{D}	$\overline{\mathcal{D}}$
$\overline{\mathcal{D}}$	$\overline{\mathcal{D}}$	$\overline{\mathcal{D}}$	\mathcal{D}

 

- There are a few details not explained in the pseudocode
- Signals should be selected in order to drive the frontier forward
 - Backtracking is the action of backing up and taking the closest previously unexplored branch in the decision tree

D-algorithm example

 

AND D-cubes of propagation

input		AND
a	b	z
1	\mathcal{D}	\mathcal{D}
1	$\overline{\mathcal{D}}$	$\overline{\mathcal{D}}$
\mathcal{D}	1	\mathcal{D}
$\overline{\mathcal{D}}$	1	$\overline{\mathcal{D}}$
\mathcal{D}	\mathcal{D}	\mathcal{D}
$\overline{\mathcal{D}}$	$\overline{\mathcal{D}}$	$\overline{\mathcal{D}}$

NOR D-cubes of failure

gate	detection input		D-cube of failure			
	a	b	z	a	b	z
NOR	0	0	s-a-0	0	0	\mathcal{D}
	0	1	s-a-1	0	1	$\overline{\mathcal{D}}$
	1	0	s-a-1	1	0	\mathcal{D}
	1	1	s-a-1	1	1	$\overline{\mathcal{D}}$

Caveats

- This lecture has only introduced some topics in testing
 - If you intend to do research in this area, take a few courses on testing
- Single stuck-at fault model is becoming obsolete

NOR D-cubes of failure

gate	detection input		D-cube of failure			
	a	b	z	a	b	z
NOR	0	0	s-a-0	0	0	\mathcal{D}
	0	1	s-a-1	0	1	$\overline{\mathcal{D}}$
	1	0	s-a-1	1	0	$\overline{\mathcal{D}}$
	1	1	s-a-1	1	1	$\overline{\mathcal{D}}$

NOR D-cubes of propagation

input		NOR
a	b	z
0	\mathcal{D}	\mathcal{D}
0	$\overline{\mathcal{D}}$	\mathcal{D}
\mathcal{D}	0	$\overline{\mathcal{D}}$
$\overline{\mathcal{D}}$	0	\mathcal{D}
\mathcal{D}	\mathcal{D}	$\overline{\mathcal{D}}$
$\overline{\mathcal{D}}$	$\overline{\mathcal{D}}$	\mathcal{D}

D-algorithm summary

- If a test for a fault exists, guaranteed to generate it
 - Full backtracking
- However, much faster than Boolean difference

Caveats

- D-algorithm is actually more complicated
 - Avoiding backtracking is important for performance
 - Implications
 - Heuristics to make best decisions first
 - Should understand derivation of D-cubes for arbitrary fault models

D-algorithm reference

Stanley Hurst. *VLSI Testing: Digital and Mixed Analogue/Digital Techniques*. Institution of Electrical Engineers, U.K., 1998

- This is one of the better references in the library
- Beware: The \mathcal{D} -algorithm examples contain small errors

45

Robert Dick

Advanced Digital Logic Design

D-algorithm review

- Given a fault, the \mathcal{D} -algorithm will generate a test for that fault
- Selects a \mathcal{D} -cube of failure to excite the fault
- Propagates a \mathcal{D} value to the circuit outputs by selection \mathcal{D} -cubes of propagation for gates
- Justifies gate inputs
- Uses full backtracking on \mathcal{D} -cubes of failure and gate justification

49

Robert Dick

Advanced Digital Logic Design

Test sequence generation

The \mathcal{D} -algorithm gives us a way to generate a test for a given fault
However, we need a sequence of tests for all (or most) faults

```
Determine all stuck-at faults for the circuit
Eliminate equivalent faults
while untested faults remain do
  Pick a fault and use an ATPG to generate a test
  Append the test to a list
  Use a fault simulator to determine all faults the test detects
  Eliminate detected faults
end while
```

51

Robert Dick

Advanced Digital Logic Design

Test sequence generation

```
while fault coverage is less than 90% do
  Generate a random pattern – extremely fast
  Use a fault simulator to determine if new faults are detected
  if so then
    Append pattern to a list
    Eliminate detected faults
  end if
end while
while fault coverage is less than 99.5% do
  Pick a fault and use an ATPG to generate a test
  Append the test to a list
  Use a fault simulator to determine all faults the test detects
  Eliminate detected faults
end while
```

53

Robert Dick

Advanced Digital Logic Design

CAD survey reference

Melvin A. Breuer, Majid Sarrafzadeh, and Fabio Somenzi.
Fundamental CAD algorithms. *IEEE Trans. Computer-Aided Design of Integrated Circuits and Systems*, 18(12):1449–1475, December 2000

- Recommended by a student
- Introduces a number of important logic-level and physical-level CAD algorithms
- A useful supplement to the material in Hachtel and Somenzi's, and Sherwani's books
- Introduces the \mathcal{D} -algorithm

46

Robert Dick

Advanced Digital Logic Design

Fault simulator

- Fault simulation is the process of determining which faults a test detects
- Test generation is complicated and time-consuming
- Fault simulation is quick

50

Robert Dick

Advanced Digital Logic Design

Test sequence generation

- However, this approach can still be too expensive
- Recall
 - Fault simulation is fast
 - ATPG is slow
- Take advantage of fault simulator

52

Robert Dick

Advanced Digital Logic Design

Redundancies

- Sometimes a s-at-0 fault can't be detected
 - Implication: Given any set of inputs to the circuit, that node can be set to 0 and the output will match the specifications
- Converse for s-a-1 faults
- Even if a portion of the circuit is not able the switch, the same function is realized
- The presence of an undetectable fault implies redundancy
- How can the \mathcal{D} -algorithm be used to simplify logic?

55

Robert Dick

Advanced Digital Logic Design

Redundancies

Logic terminating in the location of the stuck-at fault can be removed from the circuit and the same function will be realized

- Conventional wisdom suggests removal
 - Simplify logic
 - Make circuit more fully testable

ATPG for logic simplification


Can use ATPG algorithm to simplify logic

- 1 Find a fault that is untestable due to redundancy
- 2 Remove the redundant logic
- 3 Repeat


Sequential testing

- Can convert to a version of combinational testing
 - Iterative array expansion
- Simulation-based

Iterative array expansion

 

Redundancy example

 

Excite: $a \neq b$
Sensitize: $a = b = 0$
Can't excite and propagate faulty value to z!
Replace s-a-0 logic with 0
Eliminate unused logic
Simplify logic

Redundancy removal not always safe

- Logical equivalence may not imply true equivalence
- What happens if redundancy is intentional?
 - To reduce power consumption
 - To ensure signal stability for use in asynchronous circuits
- Removal can
 - Increase power
 - Introduce races

Iterative array expansion

- Make a copy of the combinational logic for each time step
- However, now the problem converts ATPG for multiple faults
- Iterative array expansion increases the size of the combinational problem
- More importantly, changes the required fault model
 - Requires ATPG for multiple faults


Modified D-algorithm for iterative array

- Propagate D-frontier forward
 - Generate new time frames as necessary
- Propagate gate justification backward
 - Generate new time frames as necessary
- However, this algorithm is not certain to find a test if one exists
 - Roth's algebra not suited to sequential circuits

Muth's 9-valued logic

- D -algorithm can't adequately model the possible states in sequential circuits
 - Repeated effect of fault can't be modeled
- Roth's values
 - 0/0, 0/1 (\bar{D}), 1/0 (D), 1/1, X/X
- Muth's values
 - 0/0, 0/1, 0/X, 1/0, 1/1, 1/X, X/0, X/1, X/X

Simulation-based sequential testing

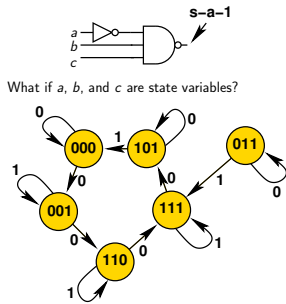

Scan-based design for test (DFT)

- If testability is considered during design or synthesis, can be made easy
- Instead of forcing ATPG to deal with synchronous testing, insert a scan chain
- Chain together (all) flip-flops and scan through an input if and only if a testing input is activated

Full scan

- Greatly simplifies testing
 - Converts sequential testing to combinational testing
- Testing can be slow if I/O pins limited
- Significantly increases chip area and price
 - More complicated flip-flops
 - More complicated routing
 - I/O requirements, especially if speed required


Simulation-based sequential testing

- Generate a vector
- Determine whether that vector brought the circuit state nearer to or farther from fault excitation and sensitization
- If the state moved near to detection, append the pattern to a list
- Many of the probabilistic optimization algorithms in the third lecture can be applied for simulation-based testing


Sequential test generation problems

- Sequential test generation **intractable** for large circuits
- Some continue to work on improving test generation
- Others modify circuit structure to make test generation easier...

Scan D flip-flop

 

Scan chain

 

Level-sensitive scan design (LSSD)

- Less delay than scan-path during normal operation
- Used commercially, especially within IBM
- Pre-processing step replaces all latches with LSSD latches
- Other companies have related testing approaches
 - Scan path – NEC
 - Scan/set – Sperry Univac
 - Random access scan – Fujitsu

Full scan disadvantages

- Increased area
 - 5%–15%
- Increased delay
 - Depends on critical path average combinational logic depth
- Slow when implemented serially
 - Need to serially clock through every register in IC
- High pin requirements to speed up

Advanced DFT/SFT techniques


- Testing core-based systems-on-chip (SoC)
 - Related to board-level boundary-scan
- Fault injection
 - Reliability evaluation
 - Insert fault into system and determine reaction
- RTL synthesis for testability
- Software fault modeling and testing
 - Extremely difficult problem

Personal observations on testing

- Companies don't want increased complexity
- Researchers want to see their ideas used
- Therefore, reduction in interest in testing among researchers
- Therefore, reduction in interest in testing among companies
- However, companies still have huge testing problems
- Therefore, high demand for MS and Ph.D. graduates with testing experience

One option: target a research problems involving testing and another area, e.g., synthesis

LSSD

 

Partial scan

- Instead of scanning all latches, scan a subset
- Need to carefully select scanned latches based on
 - Test coverage effects
 - Testing speed

Personal observations on testing

- Despite continued research on advanced testing techniques, industry continues to use full-scan
 - In order for industry to accept a more complicated testing technique, the advantages must be tremendous
 - Companies don't like complexity
- Testing is a fairly mature field
- Some people in academia have shifted their interest away from testing
 - It remains a huge practical problem for industry

Testing summary

- Low defect rate requires high test coverage
- Functional testing requires too many patterns
- Use structural testing based on a fault model, e.g., single stuck-at
- Can use fault equivalence to reduce patterns
- Can automatically generate a test for a specific fault
- Combine ATPG with fault simulator to generate a set of tests with high coverage

Testing summary

- Can use ATPG for logic simplification – redundancy
- Sequential testing difficult for large circuits
- Use DFT to make testing easier
- Use design automation to make DFT easier

Sequential testing references

- Sujit Dey, Anand Raghunathan, and Rabindra K. Roy. Considering testability during high-level design. In *Proc. Asia & South Pacific Design Automation Conf.*, February 1998
 - Survey on high-level design/synthesis for test techniques
- Kwang-Ting Cheng. Gate-level test generation for sequential circuits. *ACM Trans. Design Automation Electronic Systems*, 1(4):405–442, October 1996
 - Survey on sequential test generation