

EECS 312: Digital Integrated Circuits  
Midterm Exam

26 October 2010


Robert Dick

Show your work. Derivations are required for credit; end results are insufficient.  
Closed book. No electronic mental aids, e.g., calculators.

Honor Pledge: I have neither given nor received aid in this exam.

Signature:

 1. (15 total pts.) Consider the following figure.




- (a) (5 pts.) What type of logic gate is this?
- (b) (10 pts.) Write an expression for the total gate output node drain capacitance as a function of  $\lambda$  and constants that can be found in Section 1. Note that the transistors are all minimal-length, i.e.,  $L = 2\lambda$ . You needn't do numerical calculation. You just need to

write the expression in terms of the relevant variables. Note,  $V_{CC}$  is the system's high voltage. To those of you who already know about the Miller effect, you need not consider it in this problem. Unless you are very good at measuring, you had better show your work, e.g., by indicating your length estimates before computing capacitances based on them.

2. **(10 total pts.)** Consider the following equation for some sort of power consumption in an integrated circuit:

$$P_i = C \cdot V_{DD}^2 \cdot f \cdot A.$$

 - (a) **(2 pts.)** Use at most two sentences to explain what type of power consumption this equation models.
- (b) **(4 pts.)** Use at most one sentence to define  $C$  in this equation. A single-word definition would be insufficient.
- (c) **(4 pts.)** Use at most two sentences to describe how  $C$  might be reduced.
3. **(10 total pts.)** Consider the following transfer curve.



- (a) **(2 pts.)** What type of device is this?
- (b) **(4 pts.)** What are its  $NM_H$  and  $NM_L$ ?
- (c) **(4 pts.)** What is its  $V_M$  and  $g$  (gain)?

4. **(10 pts.)** Use three or fewer sentences to describe the properties of CMOS devices that prevented their earlier widespread use? I.e., why did BJTs long remain dominant for use in digital logic?
5. **(10 total pts.)** Draw a side view of a PMOSFET.
- (4 pts.)** Label each region with the type of material used.
  - (3 pts.)** Label the source, drain, gate, and bulk terminals.
  - (3 pts.)** Indicate any diodes in the structure.
6. **(5 pts.)** Use at most one sentence to describe why an extremely low  $V_{DD}$  can result in a higher energy consumption for a particular task than a higher, but still sub-threshold,  $V_{DD}$ .
7. **(10 pts.)** If an NMOSFET gate's dielectric were changed from  $\text{SiO}_2$  to a low- $\kappa$  material with half the permittivity of  $\text{SiO}_2$ , what would happen to its  $I_D$ ? You may assume that the NMOSFET is not velocity saturated, and that its  $V_{GS} \geq V_{TN}$ . State any assumptions and provide evidence for your answer, e.g., by writing the applicable expression for  $I_D$ .
8. **(10 total pts.) (7 pts.)** List the following interconnect fabrication steps in chronological order:
- Etch metal.
  - Expose photoresist using mask.
  - Remove all photoresist.
  - Deposit photoresist.
  - Deposit metal everywhere.
- (3 pts.)** What type of metal is this process appropriate for?

## 1 Reference material

|      | $C_{OX}$<br>(fF/ $\mu\text{m}^2$ ) | $C_O$<br>(fF/ $\mu\text{m}$ ) | $C_j$<br>(fF/ $\mu\text{m}^2$ ) | $m_j$ | $\phi_b$<br>(V) | $C_{jsw}$<br>(fF/ $\mu\text{m}$ ) | $m_{jsw}$ | $\phi_{bsw}$<br>(V) |
|------|------------------------------------|-------------------------------|---------------------------------|-------|-----------------|-----------------------------------|-----------|---------------------|
| NMOS | 6                                  | 0.31                          | 2                               | 0.5   | 0.9             | 0.28                              | 0.44      | 0.9                 |
| PMOS | 6                                  | 0.27                          | 1.9                             | 0.48  | 0.9             | 0.22                              | 0.32      | 0.9                 |

# MODELS FOR CMOS DEVICES

## CMOS (0.25 $\mu\text{m}$ ) – Unified Model.

|      | $V_{T0}$ (V) | $\gamma$ ( $\text{V}^{0.5}$ ) | $V_{DSAT}$ (V) | $k'$ ( $\text{A}/\text{V}^2$ ) | $\lambda$ ( $\text{V}^{-1}$ ) |
|------|--------------|-------------------------------|----------------|--------------------------------|-------------------------------|
| NMOS | 0.43         | 0.4                           | 0.63           | $115 \times 10^{-6}$           | 0.06                          |
| PMOS | -0.4         | -0.4                          | -1             | $-30 \times 10^{-6}$           | -0.1                          |

## CMOS (0.25 $\mu\text{m}$ ) – Switch Model ( $R_{eq}$ )

| $V_{DD}$ (V)              | 1   | 1.5 | 2  | 2.5 |
|---------------------------|-----|-----|----|-----|
| NMOS ( $\text{k}\Omega$ ) | 35  | 19  | 15 | 13  |
| PMOS ( $\text{k}\Omega$ ) | 115 | 55  | 38 | 31  |

## CMOS (0.25 $\mu\text{m}$ ) – BSIM Model

See Website: <http://bwrc.eecs.berkeley.edu/IcBook>

| Name                        | Value       |
|-----------------------------|-------------|
| $kT/q$                      | 25.875 mJ/C |
| NMOSFET $I_S$               | 21.0 pA     |
| PMOSFET $I_S$               | 41.8 pA     |
| $n$ (for $I_D$ calculation) | 1.5         |

# VALUES OF MATERIAL AND PHYSICAL CONSTANTS

| Name  | Symbol          | Value                  | Units                       |
|---|-----------------|------------------------|-----------------------------|
| Room temperature  | $T$             | 300 (= 27°C)           | K                           |
| Boltzman constant   | $k$             | $1.38 \times 10^{-23}$ | J/K                         |
| Electron charge   | $q$             | $1.6 \times 10^{-19}$  | C                           |
| Thermal voltage   | $\phi_T = kT/q$ | 26                     | mV (at 300 K)               |
| Intrinsic Carrier Concentration (Silicon)                     | $n_i$           | $1.5 \times 10^{10}$   | $\text{cm}^{-3}$ (at 300 K) |
| Permittivity of Si  | $\epsilon_{si}$ | $1.05 \times 10^{-12}$ | F/cm                        |
| Permittivity of $\text{SiO}_2$                                | $\epsilon_{si}$ | $3.5 \times 10^{-13}$  | F/cm                        |
| Resistivity of Al   | $\rho_{Al}$     | $2.7 \times 10^{-8}$   | $\Omega\text{-m}$           |
| Resistivity of Cu   | $\rho_{Cu}$     | $1.7 \times 10^{-8}$   | $\Omega\text{-m}$           |
| Magnetic permeability of vacuum (similar for $\text{SiO}_2$ ) | $\mu_0$         | $12.6 \times 10^{-7}$  | Wb/Am                       |
| Speed of light (in vacuum)                                    | $c_0$           | 30                     | cm/nsec                     |
| Speed of light (in $\text{SiO}_2$ )                           | $c_{01}$        | 15                     | cm/nsec                     |

# FORMULAS AND EQUATIONS

## Diode

$$I_D = I_S(e^{V_D/\phi_T} - 1) = Q_D/\tau_T$$

$$C_j = \frac{C_{j0}}{(1 - V_D/\phi_0)^m}$$

$$K_{eq} = \frac{-\phi_0^m}{(V_{high} - V_{low})(1 - m)} \times \frac{1}{[(\phi_0 - V_{high})^{1-m} - (\phi_0 - V_{low})^{1-m}]}$$

## MOS Transistor

$$V_T = V_{T0} + \gamma(\sqrt{|-2\phi_F + V_{SB}|} - \sqrt{|-2\phi_F|})$$

$$I_D = \frac{k_n W}{2L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS}) \text{ (sat)}$$

$$I_D = v_{sat} C_{ox} W \left( V_{GS} - V_T - \frac{V_{DSAT}}{2} \right) (1 + \lambda V_{DS}) \text{ (velocity sat)}$$

$$I_D = k_n \frac{W}{L} (V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \text{ (triode)}$$

$$I_D = I_S e^{\frac{V_{GS}}{n k T / q}} \left( 1 - e^{-\frac{V_{DS}}{k T / q}} \right) \text{ (subthreshold)}$$

## Deep Submicron MOS Unified Model

$$I_D = 0 \text{ for } V_{GT} \leq 0$$

$$I_D = k' \frac{W}{L} \left( V_{GT} V_{min} - \frac{V_{min}^2}{2} \right) (1 + \lambda V_{DS}) \text{ for } V_{GT} \geq 0$$

$$\text{with } V_{min} = \min(V_{GT}, V_{DS}, V_{DSAT})$$

$$\text{and } V_{GT} = V_{GS} - V_T$$

## MOS Switch Model

$$R_{eq} = \frac{1}{2} \left( \frac{V_{DD}}{I_{DSAT}(1 + \lambda V_{DD})} + \frac{V_{DD}/2}{I_{DSAT}(1 + \lambda V_{DD}/2)} \right) \approx \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left( 1 - \frac{5}{6} \lambda V_{DD} \right)$$

## Inverter

$$V_{OH} = f(V_{OL})$$

$$V_{OL} = f(V_{OH})$$

$$V_M = f(V_M)$$

$$t_p = 0.69 R_{eq} C_L = \frac{C_L (V_{swing}/2)}{I_{avg}}$$

$$P_{dyn} = C_L V_{DD} V_{swing} f$$

$$P_{stat} = V_{DD} I_{DD}$$

## Static CMOS Inverter

$$V_{OH} = V_{DD}$$

$$V_{OL} = GND$$

$$V_M \approx \frac{r V_{DD}}{1 + r} \text{ with } r = \frac{k_p V_{DSATp}}{k_n V_{DSATn}}$$

$$V_{IH} = V_M - \frac{V_M}{g} \quad V_{IL} = V_M + \frac{V_{DD} - V_M}{g}$$

$$\text{with } g \approx \frac{1 + r}{(V_M - V_{Tn} - V_{DSATn}/2)(\lambda_n - \lambda_p)}$$

$$t_p = \frac{t_{pHL} + t_{pLH}}{2} = 0.69 C_L \left( \frac{R_{eqn} + R_{eqp}}{2} \right)$$

$$P_{av} = C_L V_{DD}^2 f$$

## Interconnect

$$\text{Lumped RC: } t_p = 0.69 RC$$

$$\text{Distributed RC: } t_p = 0.38 RC$$

RC-chain:

$$\tau_N = \sum_{i=1}^N R_i \sum_{j=i}^N C_j = \sum_{i=1}^N C_i \sum_{j=1}^i R_j$$

Transmission line reflection:

$$\rho = \frac{V_{refl}}{V_{inc}} = \frac{I_{refl}}{I_{inc}} = \frac{R - Z_0}{R + Z_0}$$

# CMOS COMBINATIONAL LOGIC

## Transistor Sizing using Logical Effort

$$F = \frac{C_L}{C_{g1}} = \prod_1^N \frac{f_i}{b_i} \quad G = \prod_1^N g_i \quad D = t_{p0} \sum_{j=1}^N \left( p_j + \frac{f_j g_j}{\gamma} \right)$$

$$B = \prod_1^N b_i \quad H = FGB \quad D_{min} = t_{p0} \left( \sum_{j=1}^N p_j + \frac{N(N/H)}{\gamma} \right)$$