

EECS 312 Homework 2 Solution

Q1:


Plasma Etching is more selective (directional etching, anisotropic) compared to wet etching (isotropic) however wet etching can be performed in batch mode (processing many wafers all at once).

Q3:

By using the high k dielectric and keeping all the other parameters constant we can increase transconductance compared to the case with a low k dielectric material. $I \sim C_{ox}$ and $C_{ox} = \epsilon_{ox}/t_{ox}$. By changing silicon dioxide (SiO₂) with a high K dielectric material, let's say y we have $I \sim C_y = \epsilon_y/T_y$ and $\epsilon_y > \epsilon_{ox}$. Therefore we have more current.

 Q4:

A double-gate transistors on an SOI substrate in which the gate is wrapped around the channel.



Q5:

In the question it says: $V_{DD} = V_t$; conclusion: this devices is either in cut off or linear region.

a) C_{gcs} , C_{gcd} and C_{gcb} contribute to C_T .


b) $V_{gs} < V_t$: Cut-off: $C_T = C_{gcb} = WLC_{ox}$

$V_{gs} - V_t < V_{ds}$: Saturation: $C_T = C_{gcs} = 2/3 WLC_{ox}$

$V_{gs} - V_t > V_{ds}$: Linear: $C_T = C_{gcs} + C_{gcd} = 1/2 WLC_{ox} + 1/2 WLC_{ox} = WLC_{ox}$

c) $t = t_1 + t_2 = C_1 \Delta V_1 / I_{in} + C_2 \Delta V_2 / I_{in} = WLC_{ox} \cdot V_t / I_{in} + 2/3 \cdot WLC_{ox} \cdot (2V_t - V_t) / I_{in} + WLC_{ox} \cdot (3V_t - 2V_t) / I_{in}$
 $= 8/3 \cdot WLC_{ox} \cdot V_t / I_{in}$

Q6:

 

$$V_{tA} = -0.4V \quad V_{DD} = 2.5V$$

(a) $V_{in} = 0V$; this implies B is off

No current flows through A, but is on since $V_{GS} = 0 > -0.4V$

The mode of operation of A is linear as $V_{GS} - V_t > V_{DS} = 0V$

($V_{out} = 2.5V$ as it pulled to VDD)

(b) $V_{in} = 2.5V$ and B is on

(i) First assume both A and B is in linear region:

$$I_D = k_n' W/L [(V_{GS} - V_t)V_{DS} - V_{DS}^2/2]$$

Setting two current in two devices equal:

$$k_n' W/L [(V_{GS_B} - V_{t_B})V_{DS_B} - V_{DS_B}^2/2] = k_n' W/L [(V_{GS_A} - V_{t_A})V_{DS_A} - V_{DS_A}^2/2]$$

$$(2.5 - 0.4)V_{out} - V_{out}^2/2 = 0.4(2.5 - V_{out}) - (2.5 - V_{out})^2/2$$

→ Doesn't solve

(ii) Assume B is in saturation while A is in linear:

$$\frac{1}{2} k_n' W/L (V_{GS_B} - V_{t_B})^2 = k_n' W/L [(V_{GS_A} - V_{t_A})V_{DS_A} - V_{DS_A}^2/2]$$

$$\frac{1}{2} (2.5 - 0.4)^2 = 0.4(2.5 - V_{out}) - (2.5 - V_{out})^2/2$$

$V_{out} = 2.1 + 2.062i$, $2.1 + 2.062i$ → Complex, Not good.

(iii) Assume B is in linear while A is in saturation:

$$k_n' W/L [(V_{GS_B} - V_{t_B})V_{DS_B} - V_{DS_B}^2/2] = \frac{1}{2} k_n' W/L (V_{GS_A} - V_{t_A})^2$$

$$(2.5 - 0.4)V_{out} - V_{out}^2/2 = \frac{1}{2} (0.4)^2$$

$$V_{out} = 0.038V, 4.16V (> V_{DD})$$

Check B is in linear: $2.5 - 0.038 > V_t$ → o.k.

Check A is in saturation: $0 - (2.5 - 0.038) < V_t$ → o.k.

(c) $P_{avg} = 2.5V \cdot I_D \cdot 0.7 (V_{in} = 2.5V) + 2.5V \cdot 0 \cdot 0.3 (V_{in} = 0V)$
 $= 2.5V \cdot (\frac{1}{2} k_n' W/L (0.4)^2) \cdot 0.7 = 0.14 \cdot k_n' \cdot W/L \text{ Watt}$

Q7:

(a) $P_{dynamic} = CV^2 f_{0 \rightarrow 1}$


$$P_{clock} = 10000 \cdot 40fF \cdot 2.5V^2 \cdot 1GHz = 2.5W$$

$$P_{comb} = 5000000 \cdot 6fF \cdot 2.5V^2 \cdot (0.1 \cdot 1GHz \cdot 0.5) = 9.375W \rightarrow f_{0 \rightarrow 1} = \alpha_{sw} \cdot 1GHz \cdot 0.5$$

$$P_{\text{dynamic}} = P_{\text{clock}} + P_{\text{comb}} = 11.875\text{W}$$

$$\text{Time}_{\text{depletion}} = E_{\text{battery}} / P_{\text{dynamic}} = 39\text{W}\cdot\text{hr} / 11.875\text{W} = 3.28\text{ hours}$$

 - (b) $I_{\text{off}} (I_{\text{DS}} @ V_{\text{GS}}=0)$ is given as 10^{-10}A for $V_t=0.5\text{V}$
Determine I_{off} when $V_t=0.25\text{V}$



Note that V_t shift corresponds with a shift of I_{DS} vs. V_{GS} graph

Slope of sub-threshold region is 90 mV/dec and shifting the sub-threshold line left by 250mV will increase the off current by $250\text{mV}/90\text{mV} = 2.78\text{dec}$

$$\text{Therefore } I_{\text{off}} @ V_t=0.25\text{V} = 10^{-10} \cdot 10^{2.78} = 10^{-7.22} = 6.026 \cdot 10^{-8}\text{A}$$

$$P_{\text{static}} = I_{\text{static}} \cdot V = 5010000 \cdot 6.026 \cdot 10^{-8}\text{A} \cdot 2.5\text{V} = 0.75\text{W}$$

$$P_{\text{total}} = P_{\text{dynamic}} + P_{\text{static}} = 11.875\text{W} + 0.75\text{W} = 12.625\text{W}$$

$$\text{Time}_{\text{depletion}} = E_{\text{battery}} / P_{\text{total}} = 39\text{W}\cdot\text{hr} / 12.625\text{W} = 3.09\text{ hours}$$

$$\% \text{ reduction} = (3.28 - 3.09) / 3.28 = 5.79\%$$

- (C) From Fig. 5-17 @ $V_{\text{DD}}=1.3$ normalized t_p is ~ 2 . That is, propagation delay has doubled so peak frequency has to be halved. The operating clock frequency = $0.5 \cdot 1\text{GHz} = 500\text{MHz}$

$$P_{\text{dynamic}} = P_{\text{clock}} + P_{\text{comb}} = 10000 \cdot 40\text{fF} \cdot 1.3\text{V}^2 \cdot 500\text{MHz} + 5000000 \cdot 6\text{fF} \cdot 1.3\text{V}^2 \cdot 0.10 \cdot 500\text{MHz} \cdot 0.5 = 1.61\text{W}$$

$$P_{\text{static}} = 5010000 \cdot 6.026 \cdot 10^{-8}\text{A} \cdot 1.3\text{V} = 0.391\text{W}$$

$$P_{\text{total}} = P_{\text{dynamic}} + P_{\text{static}} = 2.00\text{W}$$

$$\text{Time}_{\text{depletion}} = E_{\text{battery}} / P_{\text{total}} = 39\text{W}\cdot\text{hr} / 2\text{W} = 19.5\text{ hours}$$

- (d) $P_{\text{dynamic}} = P_{\text{clock}} + P_{\text{comb}} = 10000 \cdot 40\text{fF} \cdot 2.5\text{V}^2 \cdot 500\text{MHz} + 5000000 \cdot 6\text{fF} \cdot 2.5\text{V}^2 \cdot 0.10 \cdot 500\text{MHz} \cdot 0.5 = 5.94\text{W}$

$$P_{\text{static}} = 5010000 \cdot 6.026 \cdot 10^{-8}\text{A} \cdot 2.5\text{V} = 0.75\text{W}$$

$$P_{\text{total}} = P_{\text{dynamic}} + P_{\text{static}} = 6.69\text{W}$$

$$\text{Time}_{\text{depletion}} = E_{\text{battery}} / P_{\text{total}} = 39\text{W}\cdot\text{hr} / 6.69\text{W} = 5.83\text{ hours}$$

Q10:

$$V_{\text{instantaneous}} = V_{\text{final}} + (V_{\text{initial}} - V_{\text{final}}) e^{-t/RC}$$

- (a) By replacing the PMOSFET with $3.8\text{k}\Omega$,

$$V_{\text{DD}}/2 = 0 - (V_{\text{DD}} - 0) e^{-t/3.8\text{k}\Omega \cdot 73.2\text{fF}}$$

$$t = \ln 2 \cdot 3.8\text{k}\Omega \cdot 73.2\text{fF} = 0.693 \cdot 2.782 \cdot 10^{-10} = 192.81\text{ps}$$

- (b) PMOSFET will be cut-off when $V_{GS} > V_t$ and for a PMOSFET, the terminal with the higher voltage is source between source and drain terminals. In this problem, the terminal connected to C_L will have the higher voltage, so it works as a source terminal.

The PMOSFET will continue to discharge the C_L , but if C_L is discharged to $|V_{TP}|=0.5V$, the PMOSFET will be cut-off since $V_{GS}=0-V_S=-V_{CL} > V_t=-0.5V$
Therefore the final voltage of the capacitor is $|V_{TP}|=0.5V$

- (c) Since we assumed resistor-switch model, the final voltage is still 0. In this equation, we assume there is a sudden change in resistance to infinity when PMOS cuts-off.

$$0.5 = 0 - (V_{DD} - 0) e^{-t/3.8k\Omega \cdot 73.2fF}$$

$$t = \ln 5 \cdot 3.8k\Omega \cdot 73.2fF = 0.693 \cdot 2.782 \cdot 10^{-10} = 447.68ps$$

- (d) Resistor-switch model assumes a constant resistance (3.8K Ω) during a transition before cut-off and a step change in resistance to infinity as the PMOSFET becomes cut-off. However, with a real PMOSFET, on-resistance increases gradually with decreasing $|V_{GS}|$. Since R is a function of time that is monotonically increasing, RC time constant and delay will increase over a transition. Therefore, the delay calculated with resistor-switch model may be optimistic. i.e., with a real PMOSFET, it takes more time to get to the final voltage due to long tailed transition.