

Homework Four

EECS 312: Digital Integrated Circuits

Teacher: Robert Dick
Assigned: 8 November
Due: 20 November

You may discuss the assignment with your classmates. However, you need to understand and write the solutions independently.

1. (10 pts.) Show the circuit diagram for


$$f(a, b, c) = ab + \bar{a}\bar{b}\bar{c} \quad (1)$$

implemented with


- (a) (5 pts.) Transmission gates (with output buffer or inverter) and
- (b) (5 pts.) Pass transistors (with output buffer or inverter).

Do not assume access to complemented input literals.

 2. (10 pts.) In the latch in the following figure, compute the setup time when D is low (that is, a low value is being passed from D to X). Assume the initial voltage at node X is $(V_{DD} - V_{Tn}(V_x)) = 1.8\text{ V}$. You must compute the equivalent resistance of the pass transistor at the midpoint of the voltage swing of interest. Let the width of the NMOS pass transistor be $W=1\ \mu\text{m}$ and the PMOS/NMOS sizes of the inverter are $2\ \mu\text{m}$ and $1\ \mu\text{m}$ respectively. Assume that the junction+sidewall capacitance is $0.6\ \text{fF}/\mu\text{m}$ multiplied by the transistor width and ignore overlap capacitance.




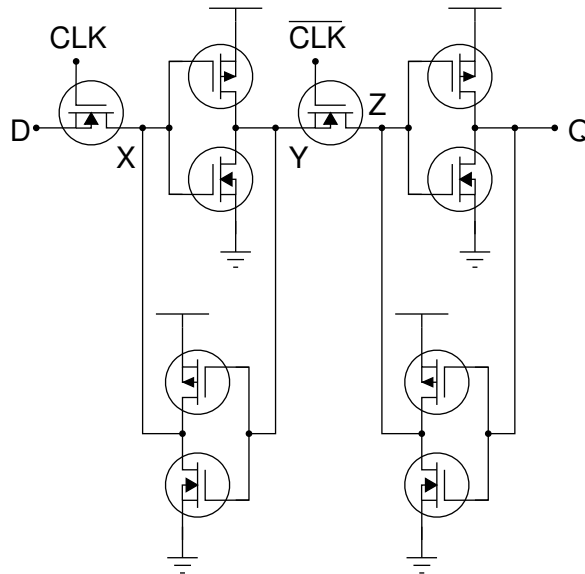3. (15 total pts.) Assume the register shown below is driven at input D by a CMOS inverter. 4 cross-coupled inverters in the flip-flop have $W_p=W_n=0.5\ \mu\text{m}$ and minimum channel length.



 - (a) **(7 pts.)** Find an inequality relationship among the width of the pass transistor connected to node X, the width of the (off-diagram) inverter driving that pass transistor, and the width of the appropriate transistor in the inverter driving node X that ensures proper functionality for storing a 0 (ignore body effect) at Q. You may need to make some simplifying assumptions regarding feedback; please describe these clearly in your answer. Take the switching voltage, $V_M = 1\text{ V}$ for the inverters with $W_p = W_n$ and the default technology parameters.
- (b) **(4 pts.)** How would you redesign the flip-flop to relax the sizing requirement on the driving stage? A qualitative answer is sufficient.
- (c) **(4 pts.)** Suppose we change the circuit by adding a feedback NMOS pass transistor inserted between the output of the feedback inverter in the leading stage and node X (the leading stage now looks like Figure 7-8a of the text). How does this change the sizing requirement of part (a)? A qualitative answer is sufficient.
4. **(10 pts.)** To perform a certain function in a microprocessor, data must propagate through 100 stages of logic, each having a delay equal to that of an inverter, t_{inv} . The speed of this operation sets the clock frequency of the system.
- (a) **(7 pts.)** Compare the speed (quantified by maximum clock frequency) of a non-pipelined system to that of a pipelined system with 10 stages. Let the design use registers having a delay equal to $3t_{inv}$ and a set-up time of $3t_{inv}$ also.
- (b) **(3 pts.)** What do the results imply about breaking up operations into an increasing number of very small operations?
5. **(10 pts.)** Given the following clock and data waveforms, draw the output waveforms for a
- (a) positive edge-triggered register and
- (b) a negative latch.

The timing characteristics of these sequential elements follow: $t_{c \rightarrow Q} = 4$ units, $t_{D \rightarrow Q} = 3$ units, $t_{setup} = t_{hold} = 2$ units. Vertical dashed lines have a separation of one unit. Note the clock period is equal to 24 units. Clearly mark on the figure where setup and hold time violations occur for each sequential element.



6. (10 total pts.) Consider a CMOS inverter driving a latch through a noisy wire. We expect noise voltage of up to 70% of V_{DD} on either supply rail to be induced in the line. We need the input to this Latch to be “clean” or noise-free.
- (3 pts.) Explain (in terms of a VTC) why a static CMOS inverter (or pair of inverters to make it non-inverting) will not be able to provide the required noise immunity if inserted before the Latch at the end of the wire.
 - (7 pts.) Suppose we place a CMOS Schmitt trigger at the end of the line, before the latch. Size the controlling inverter (M3 and M4 in Figure 7-47 of the text) to ensure proper noise rejection assuming that both the input inverter and feedback inverter have $W_p = 2\ \mu\text{m}$, $W_n = 1\ \mu\text{m}$ with minimum channel lengths.
7. (10 pts.) Demonstrate that you know how to design a 4:1 MUX from the transistor level. Your design should have a structure making it possible to be sure that the maximum resistance from an output to V_{DD} or V_{SS} is no greater than that of a balanced, minimum-width inverter. You may size relative to w , the minimal width of a FET.
8. (5 pts.) What is the state of an asynchronous finite state machine the function of? What is the output of an asynchronous finite state machine the function of?
9. (10 pts.) Design a one-input circuit that will produce a constant output when its input is 0 and will produce an output that oscillates between 0 and 1 when its input is 1. Design and size this device such that the period of oscillation is approximately 5 ns. Use transistors to supply any required resistance and capacitance.
10. (10 pts.) Consider the dynamic gate shown in the following figure. Based on the input signal, draw the output signal.

