

# EECS 312 Discussion 10

11/8


Shengshuo Lu  
(luss@umich.edu)

# Overview

- Reminder
  - Hw 4: Due Nov 16
- Dynamic Logic
- Sequential Logic

# Dynamic Logic Families


# Basic Domino gate

 


- Divide the clock in 2 phases:
  - Precharge
    - Output Low
    - Dyn. Cap precharge
    - PDN Off
  - Evaluate
    - Conditional discharge
    - Input must be stable and monotonic L→H

# Domino / Static $C_{in}/C_{out}$

3-input OR gate

 


Static:  
 $C_i = 7$   
 $C_n = 9$

 

Dynamic:  
 $C_i = 2$   
 $C_n = 7$

Skew for eval!


# Basic Domino gate

 

## Advantages:

- Faster than CMOS
- Input capacitance is lower
- Early switch point
- Inverter  $P/N > 2$  (only rising delay important)


# Basic Domino gate

 

## Disadvantages:

- Low noise margin
- Charge sharing
- Leakage currents
- Internal capacitance charge sensitive to noise


# Issues: Leakage

 

- Dynamic node is floating during evaluation
  - Leakage current of NMOS can discharge it




# Issues: Leakage

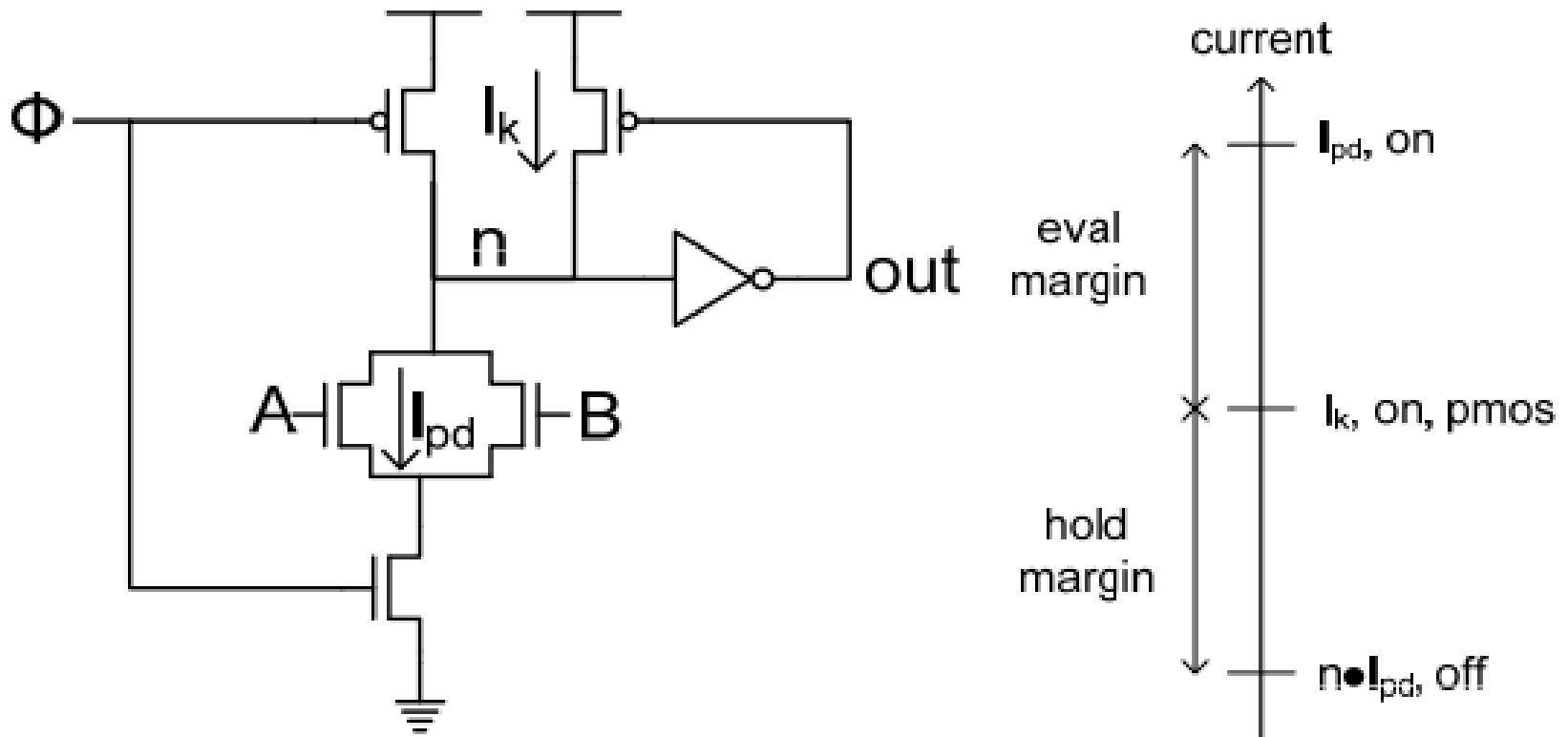



- Half latch devices:
  - Size PMOS to replenish the leakage current
  - Limits width OR gates

# Domino – with and without keeper

Graph0

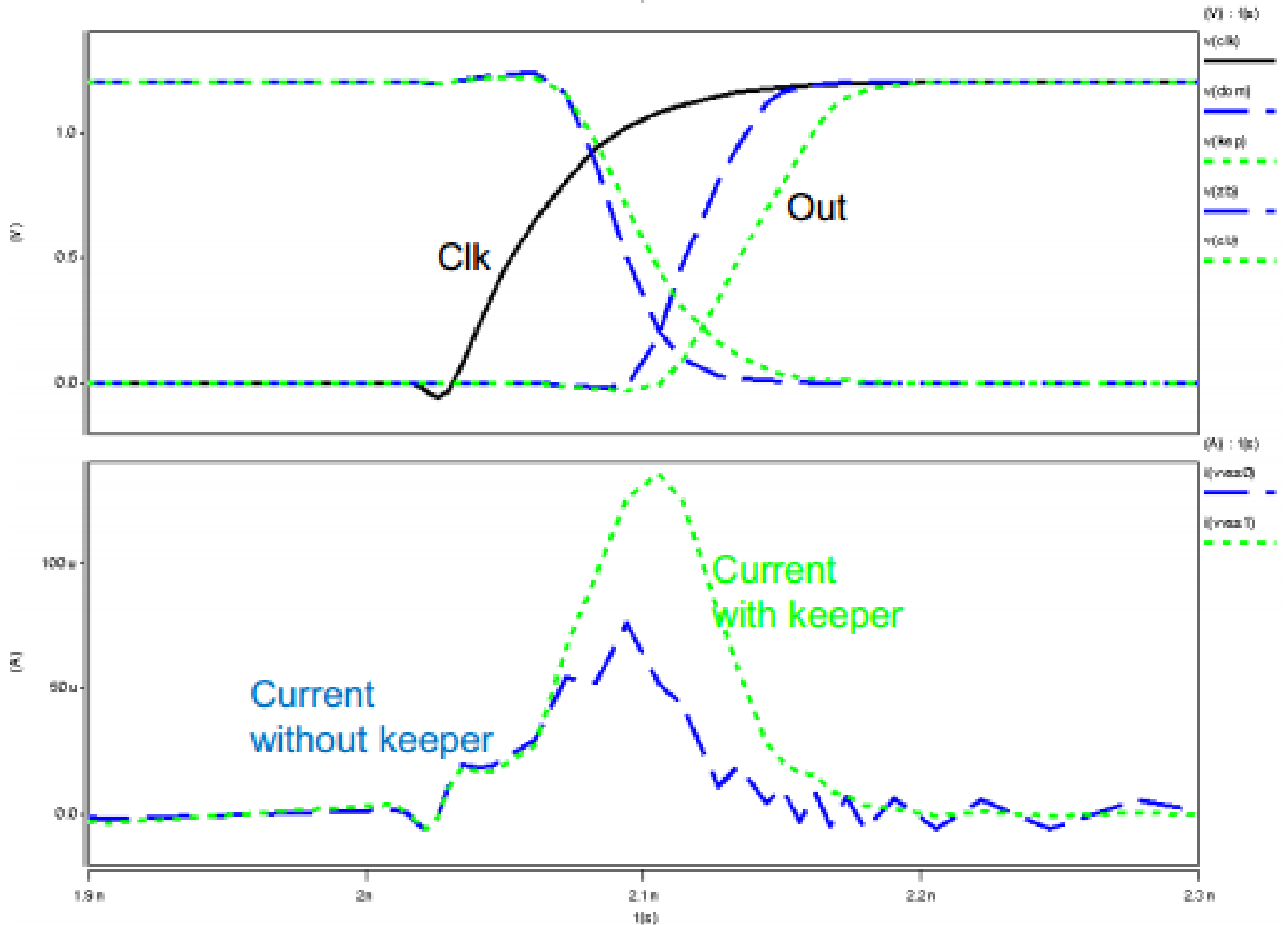


# Issues: Charge sharing

 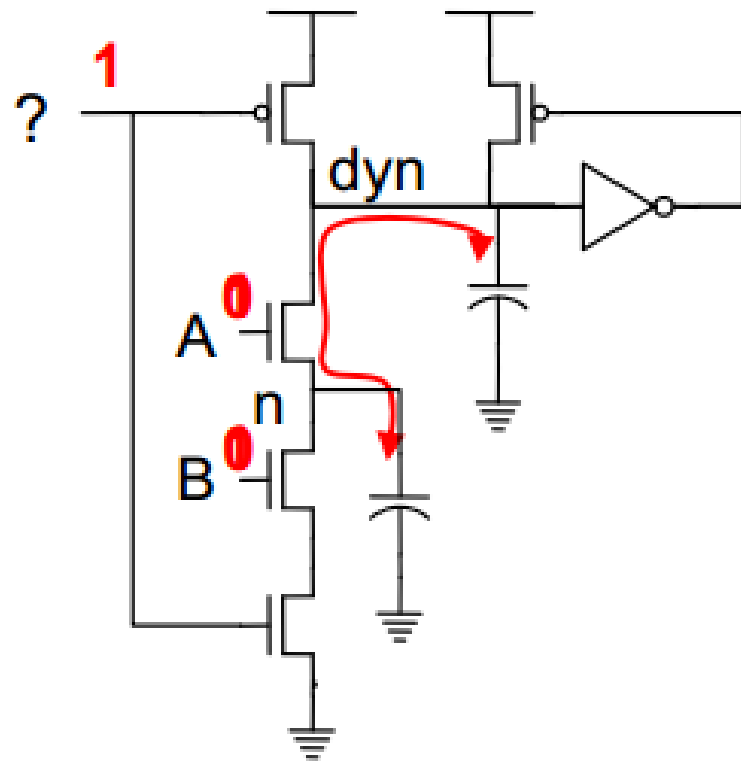


- In evaluate, dynamic node charge is shared with internal node caps
- Node was discharged in previous cycle

# Domino cascading


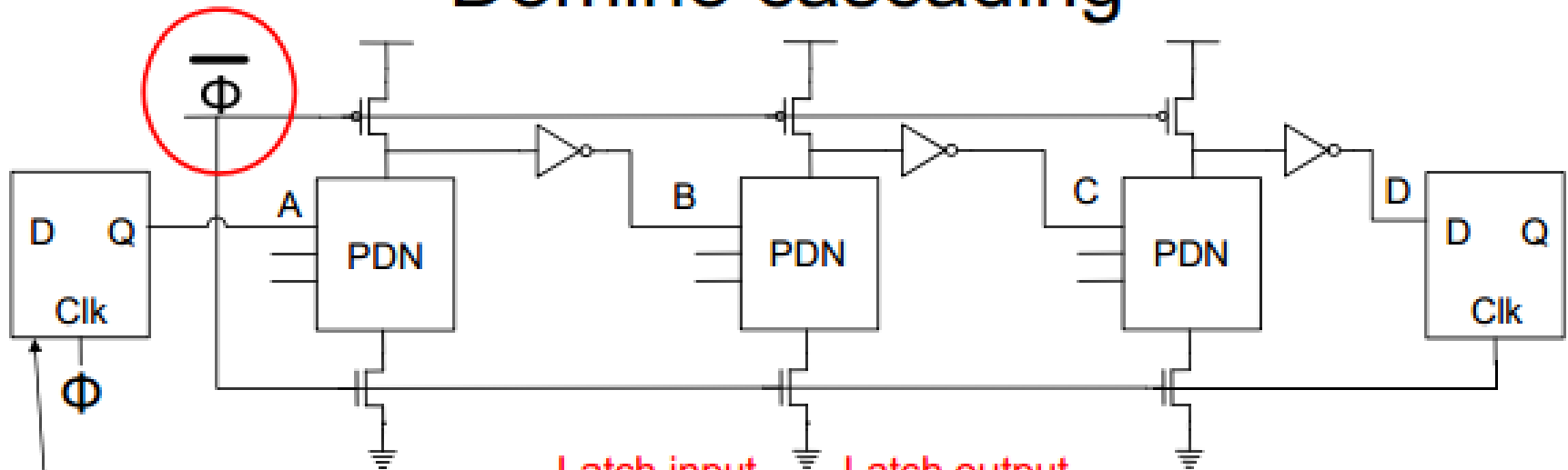


Input must be stable during eval

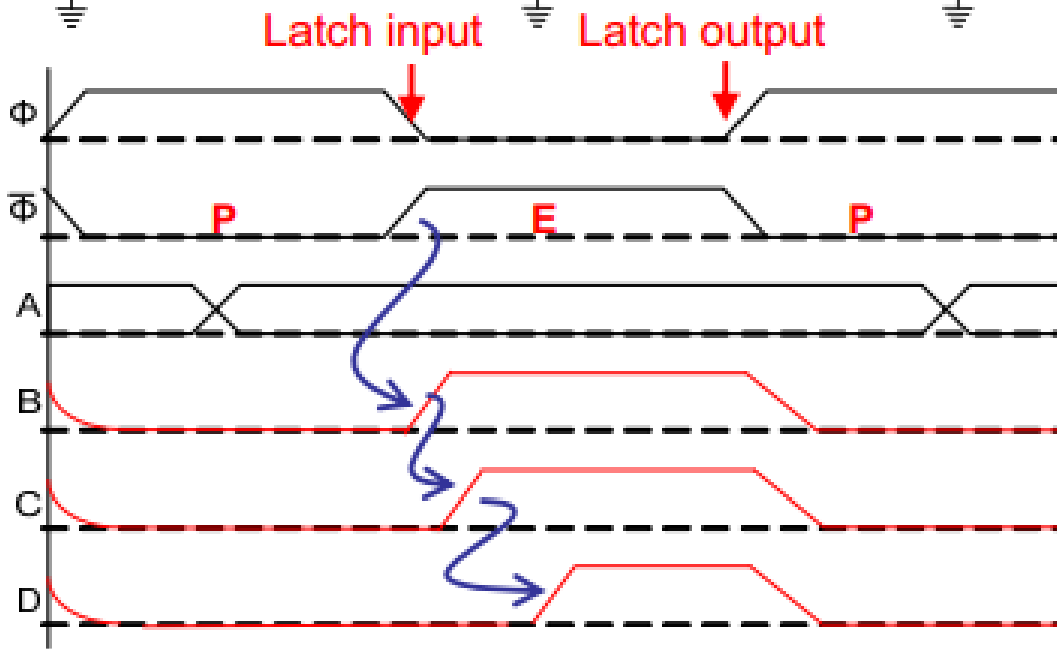


# Sequential Logic

# Flip-flop (Basics)

 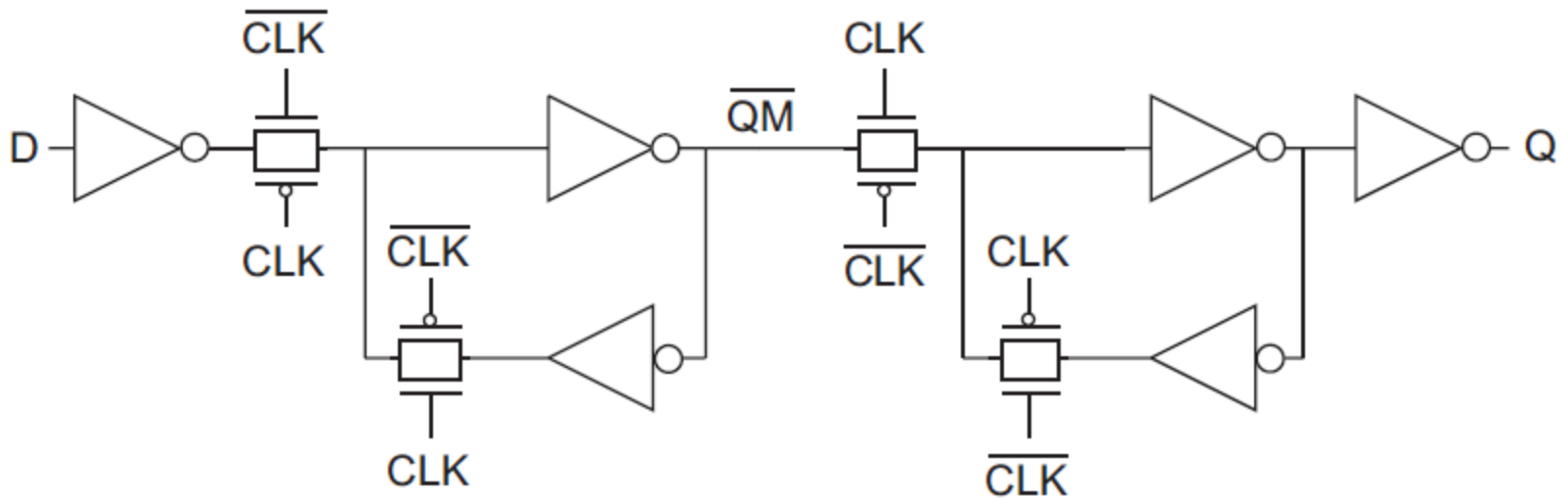

# Flip-flop


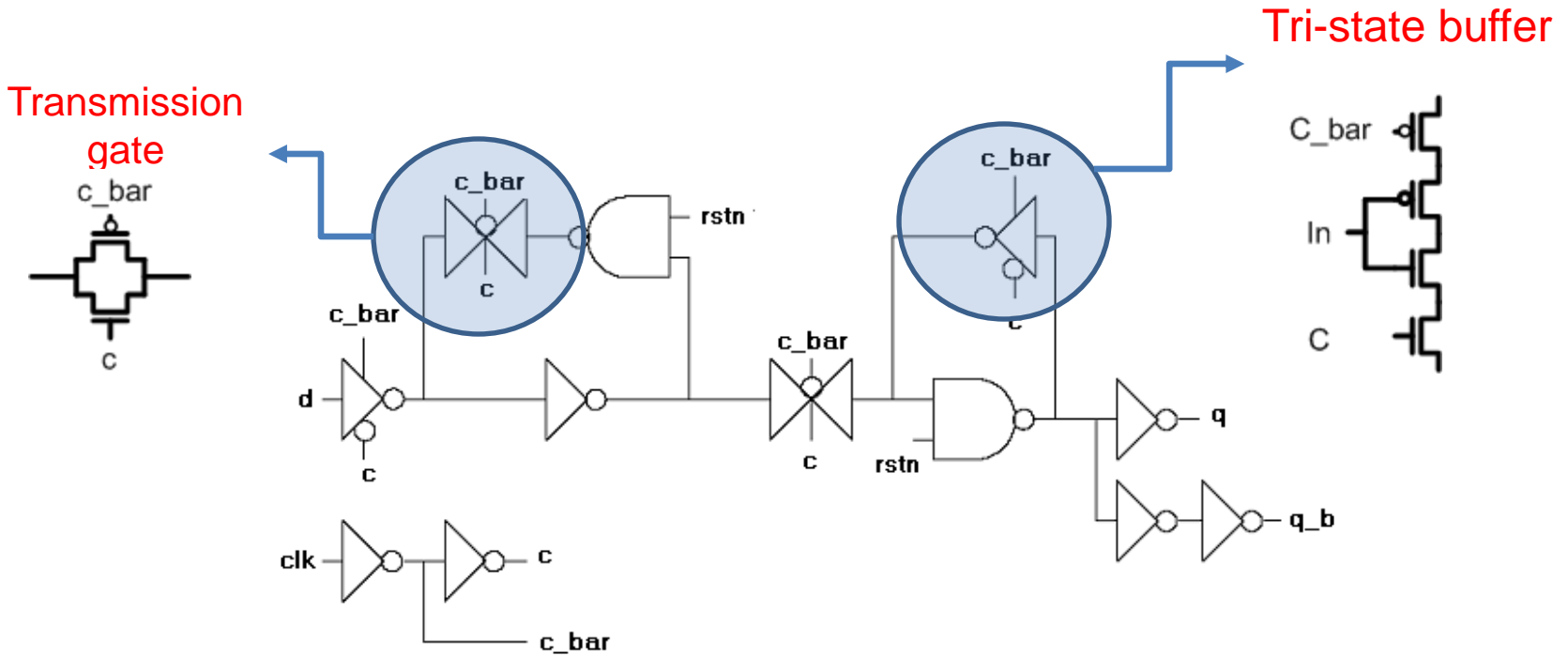


- Flip Flop with Asynchronous Reset

# Flip-flop
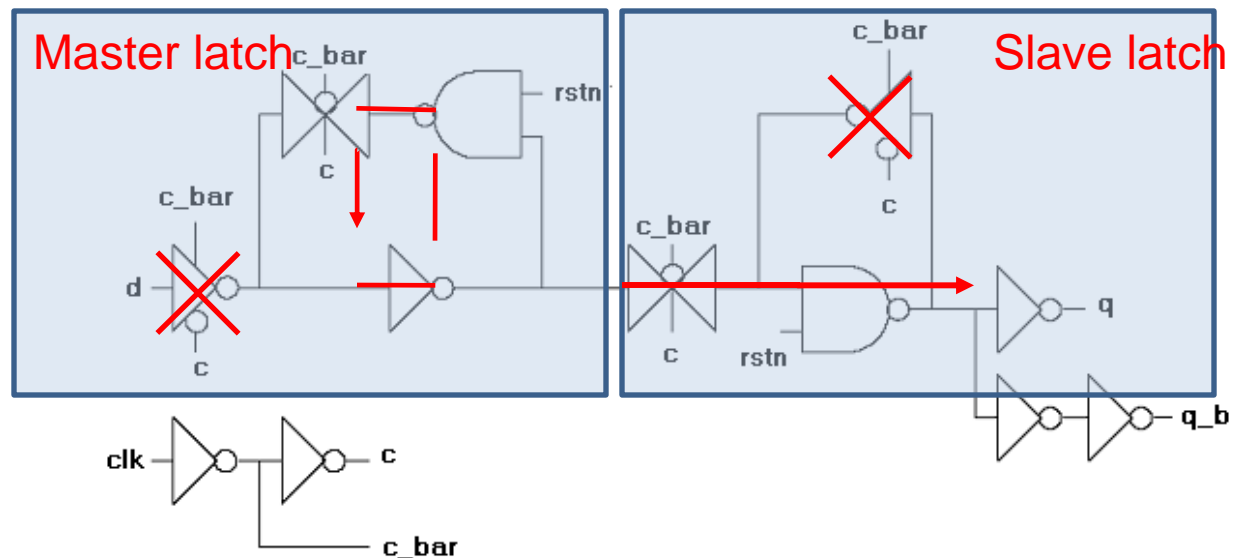 
## How it works


- Divided flip flop into 2 latches (master and slave)
- When master is transparent, slave holds.
- When master holds, slave is transparent
- Capture data at the rising edge of clock





# Flip-flop (continued)


- Important terms : C-Q delay, D-Q delay

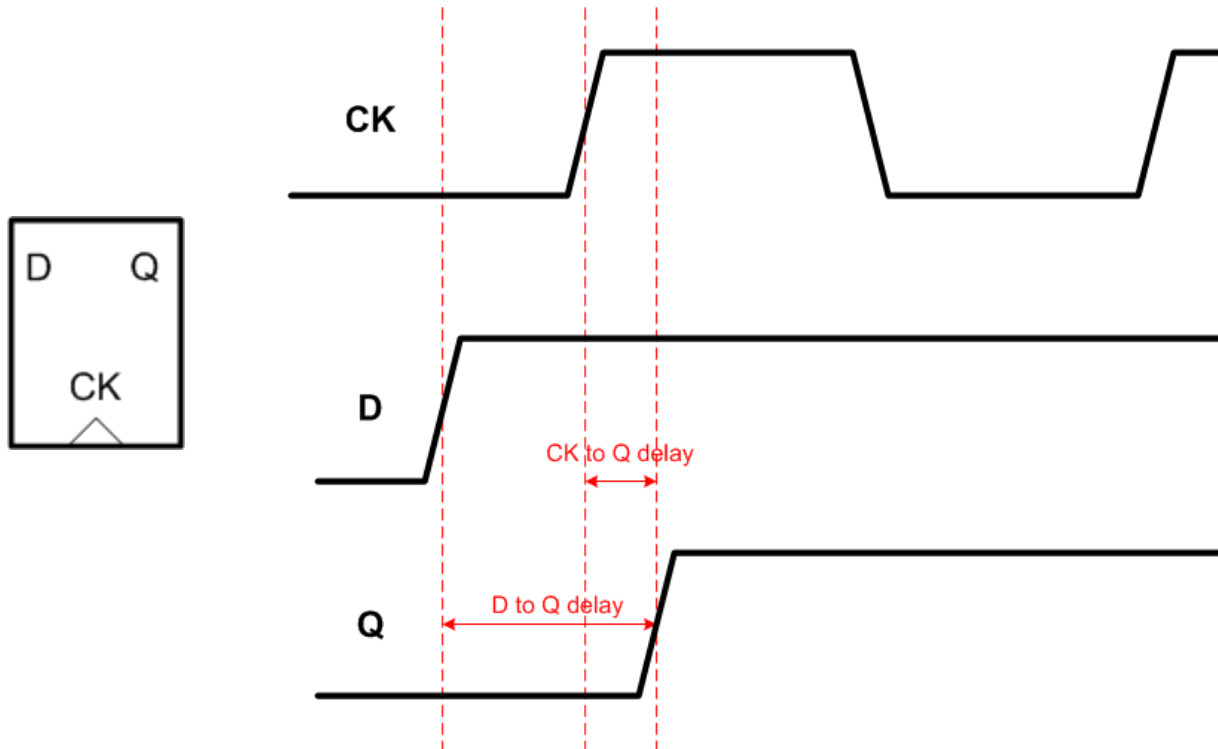
 
# Flip-flop (continued)

- Setup Time

- As D approaches to CK edge, C-Q delay goes up



When D arrives after the setup time point, we call it setup time violation

Setup-Time : Point at which CLK-Q delay rises 5% beyond nominal

# Flip-flop (continued)

- Hold Time

- Input should be stable for a period of time after the clk edge

