 


# Digital Integrated Circuits – EECS 312

<http://robertdick.org/eecs312/>

Teacher: Robert Dick      GSI: Shengshou Lu  
 Office: 2417-E EECS      Office: 2725 BBB  
 Email: dickrp@umich.edu      Email: luss@umich.edu  
 Phone: 734-763-3329  
 Cellphone: 847-530-1824



Non-idealities  
 DCVSL  
 Dynamic CMOS  
 Charge sharing  
 Homework

## Announcements

- Logical effort.
- Homework 3, problem 9 will be moved to Homework 4.
- Review DeMorgan's Laws and gate design.

2

Robert Dick

Digital Integrated Circuits

Non-idealities  
 DCVSL  
 Dynamic CMOS  
 Charge sharing  
 Homework

## Examples

- $f(a) = a$ .
- $f(a) = \bar{a}$
- $f(a, b) = \bar{a}\bar{b}$
- $f(a, b) = ab$  (Check Figure 6-33 in J. Rabaey, A. Chandrakasan, and B. Nikolic. *Digital Integrated Circuits: A Design Perspective*. Prentice-Hall, second edition, 2003!)
- $f(a, b, c) = ab + \bar{b}c$  (try both ways).

Derive and explain.

Non-idealities  
 DCVSL  
 Dynamic CMOS  
 Charge sharing  
 Homework

## Miller effect

- If  $V_D$  switches in the opposite direction of  $V_G$ , the effect of  $C_{GD}$  is doubled.
- Consider an inverter.
- Model by using a  $2C_{GD}$  capacitor to ground.


5

Robert Dick

Digital Integrated Circuits

Non-idealities  
 DCVSL  
 Dynamic CMOS  
 Charge sharing  
 Homework

## Stack effect

 


- Each series transistor drops the voltage seen by the next transistor.
- $V_T = V_{T0} + \gamma \left( \sqrt{|-2\phi_F + V_{SB}|} - \sqrt{|2\phi_F|} \right)$
- $V_{Tn2} = V_{Tn0} + \gamma \left( \sqrt{|2\phi_F + V_{int}|} - \sqrt{|2\phi_F|} \right)$

Non-idealities  
 DCVSL  
 Dynamic CMOS  
 Charge sharing  
 Homework
 
## Dynamic hazards

- Potential for two or more spurious transitions before intended transition
- Results from uneven path delays in some multi-level circuits



7


Robert Dick

Digital Integrated Circuits

Robert Dick

Digital Integrated Circuits

## Dynamic hazards

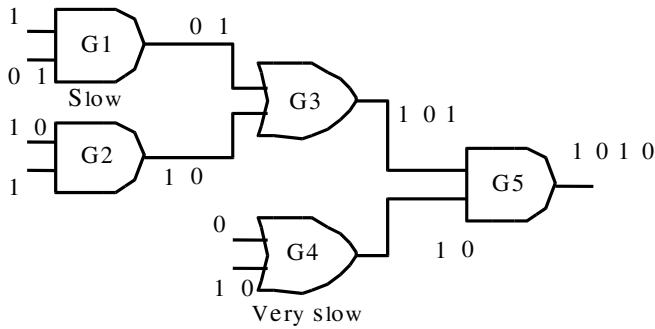


## Eliminating dynamic hazards

- Some approaches allow preservation of multi-level structure
  - Quite complicated to apply
- Simpler solution – Convert to two-level implementation
 
## Static hazards


- Still have static hazards
- Potential for transient change of output to incorrect value



## Problems with glitches

- These transitions result in incorrect output values at some times
- Also result in uselessly charging and discharging wire and gate capacitances through wire, gate, and channel resistances
  - Increase power consumption

## Glitches increase power consumption

 

## Detecting hazards

- The observable effect of a hazard is a glitch
  - A circuit that might exhibit a glitch has a hazard
- Whether or not a hazard is observed as a glitch depends on relative gate delays
- Relative gate delays change depending on a number of factors – Conditions during fabrication, temperature, age, etc.
- Best to use abstract reasoning to determine whether hazards might be observed in practice, under some conditions

## Eliminating static hazards

- Ensure that the function has a term maintaining a 0 output for all 0→0 transitions.
- Ensure that the function has a term maintaining a 1 output for all 1→1 transitions.
- There are precisely defined algorithms for this, but they build on a knowledge of logic minimization.

14

## Where do static hazards really come from?

- Static-0:  $A \bar{A}$
- Static-1:  $A + \bar{A}$
- Assume SOP form has no product terms containing a variable in complemented and uncomplemented forms
  - Reasonable assumption, if true, drop product term

15

## Where do static hazards really come from?

- Assume POS form has no sum terms containing a variable in complemented and uncomplemented forms
  - Reasonable assumption, if true, drop sum term
- Assume only one input switches at a time
- Conclusion: SOP has no 0-hazards and POS has no 1-hazards
  - In other words, if you are doing two-level design, you need not analyze the other form for hazards

16


## Living with hazards

Sometimes hazards can be tolerated

- Combinational logic whose outputs aren't observed at all times
- Synchronous systems
- Systems without tight power consumption limits


17
 
## Differential cascode voltage switch logic




19
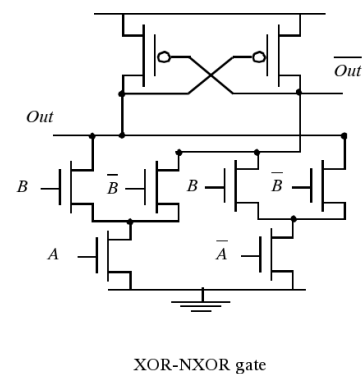
## Differential cascode voltage switch logic example




20
 
### Differential cascode voltage switch logic response




### NMOS-only wired and

 


21

22

### Level restoration

 


### Restorer sizing

 

23

24
 
### Depletion mode $V_T = 0V$ pass transistor



Consider leakage.


### Static vs. dynamic logic

- Static logic relies only on steady-state behavior of system. Eventually the output converges to a correct result.
- Dynamic logic relies on transient behavior and is sensitive to timing. Reliable design is generally trickier. Why use it?
- Static logic requires  $(k_P + k_N)$  transistors for  $k$ -input gate.
- Dynamic logic requires  $k_N + 2$  transistors for  $k$ -input gate.

25

27


## Dynamic logic

 

Two-phase operation.

28

## Dynamic logic example

 

29

## Dynamic logic operating principles I

- 1 Can only discharge output node once per clock period.
- 2 Inputs must make only one transition during evaluation.
- 3 Output can be in the high impedance state during and after evaluation.
- 4 Logic function is implemented by the pull-down network only.
- 5 Requires only  $k_N + 2$  transistors.
- 6 Full swing outputs.
- 7 Non-ratioed - sizing of the devices does not affect the logic levels.
- 8 Reduced load capacitance due to lower input capacitance.
- 9 Reduced load capacitance due to smaller output loading. no  $I_{sc}$ , so all the current provided by PDN goes into discharging  $C_L$ .

30

## Dynamic logic operating principles II

- 10 Power consumption usually higher than static CMOS.
  - Good: No static current.
  - Good: No glitching.
  - Bad: Higher transition probabilities.
  - Bad: More load on clock distribution network.
- 11  $V_M = V_{IH} = V_{IL} = V_{TN}$  so noise margin is low.
- 12 Needs precharge and evaluation cycle.

31

## Upcoming topics

- Example problems on recently covered material.
- Latches and flip-flops.

32


## Review

- What are dynamic hazards?
- What are static hazards?
- What problems do hazards cause?
- What is the root cause of static hazards?
- Let's implement a function using DCVSL.

Derive and explain.


33

## Dynamic logic charge leakage

 


35
 
## Dynamic logic charge leakage timing diagram




36

## Leakage prevention

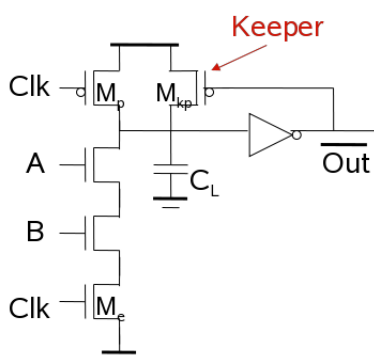


37

## Charge sharing

 

38

## Charge sharing model

 

- 1 Determine condition by setting  $\Delta V_{out} = V_{Tn}$ .
- 2 This yields  $\frac{C_a}{C_L} = \frac{V_{Tn}}{V_{DD} - V_{Tn}}$ .

39


## Charge sharing equations

$$\Delta V_{out} = \begin{cases} V_{out}^{(final)} + V_{DD} = -C_a/C_L (V_{DD} - V_{Tn}^{(V_x)}) & \text{if } \Delta V_{out} < V_{Tn} \\ -V_{DD} \frac{C_a}{C_a + C_L} & \text{if } \Delta V_{out} > V_{Tn} \end{cases}$$

Note: The book has a sign error when deriving the boundary point.


40

## Preventing charge sharing problems

 

41
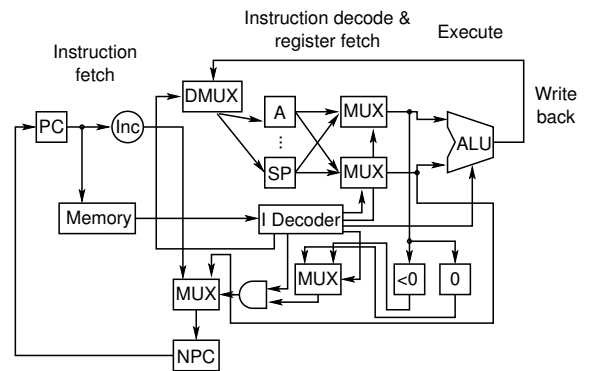
## Transition from combinational to sequential circuits



42

## Upcoming topics

- Sense amplifiers.
- A more formal approach to gate sizing.

43

## Homework assignment

- 31 October: Read Sections 6.3 and 7.1 in J. Rabaey, A. Chandrakasan, and B. Nikolic. *Digital Integrated Circuits: A Design Perspective*. Prentice-Hall, second edition, 2003.
- 7 November: Project 4.

45