

Instructor: Robert Dick
 Office: L477 Tech
 Email: dickrp@northwestern.edu
 Phone: 847-467-2298


TA: Neal Oza
 Office: Tech. Inst. L375
 Phone: 847-467-0033
 Email: nealoz@u.northwestern.edu

TT: David Bild
 Office: Tech. Inst. L470
 Phone: 847-491-2083
 Email: d-bild@northwestern.edu




NORTHWESTERN
 UNIVERSITY


Other TG diagram

 


CMOS transmission gate (TG)

 

Impact of control on input

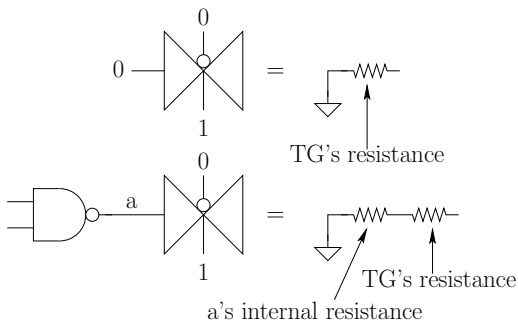

TG example

 

Two-Level Logic and Canonical Forms

- The previous example illustrated one standard representation (product of sums).
- These standard forms are known collectively as two-level logic:
 - Product of Sums (POS) e.g.

$$f = (a + \bar{b})(\bar{a} + b)$$

- Sum of Products (SOP) e.g.

$$f = \bar{a}\bar{b} + ab$$

- Can you see why these two are equivalent?
- Why is this known as two-level logic?

Practice w/ Boolean Minimization

Simplify this expression so that it has the minimal possible literal count:

$$(a + \bar{b})(\bar{a}b + cd)$$

Canonical forms - SOP

For Sum of Products (SOP) the canonical form is constructed out of *minterms*.

- Product term in which all variables appear in complemented or uncomplemented forms once
- For an n-input function corresponds to one of of 2^n possible input combinations
- Use binary representation to enumerate minterms

Canonical forms – SOP

x	y	z	term	symbol	m_0	m_1	m_2	m_3	m_4	m_5	m_6	m_7
0	0	0	$\bar{x}\bar{y}\bar{z}$	m_0	1	0	0	0	0	0	0	0
0	0	1	$\bar{x}\bar{y}z$	m_1	0	1	0	0	0	0	0	0
0	1	0	$\bar{x}yz$	m_2	0	0	1	0	0	0	0	0
0	1	1	$x\bar{y}z$	m_3	0	0	0	1	0	0	0	0
1	0	0	$x\bar{y}\bar{z}$	m_4	0	0	0	0	1	0	0	0
1	0	1	$x\bar{y}z$	m_5	0	0	0	0	0	1	0	0
1	1	0	$xy\bar{z}$	m_6	0	0	0	0	0	0	1	0
1	1	1	xyz	m_7	0	0	0	0	0	0	0	1

Canonical forms – POS

For Products of Sums (POS) the canonical form is constructed out of *maxterms*.

- Sum term in which all variables appear in complemented or uncomplemented forms once
- Use binary representation to enumerate maxterms (note: function is not true for maxterms)

Using Canonical Products of Sums Representation

Convenient representation uses \prod operator and minterms:

$$f(x_1, \dots, x_n) = \prod M_i$$

For given function f, list all maxterms for which the function is false:

$$\begin{aligned} f(a, b, c) &= (a + \bar{c})(\bar{a} + b) \\ &= M_1 \cdot M_3 \cdot M_4 \cdot M_5 \\ &= \prod M(1, 3, 4, 5) \end{aligned}$$

Logic minimization motivation

- Want to reduce area, power consumption, delay of circuits
- Hard to exactly predict circuit area from equations
- Can approximate area with SOP cubes
- Minimize number of cubes and literals in each cube
- Algebraic simplification difficult
 - Hard to guarantee optimality

Using Canonical Sum of Products Representation

Convenient representation uses \sum operator and minterms:

$$f(x_1, \dots, x_n) = \sum m_i$$

For given function f, list all minterms for which the function is true:

$$\begin{aligned} f(a, b, c) &= ab + \bar{a}\bar{c} \\ &= (m_6 + m_7) + (m_0 + m_2) \\ &= \sum m(0, 2, 6, 7) \end{aligned}$$

Canonical forms – POS

x	y	z	term	symbol	M_0	M_1	M_2	M_3	M_4	M_5	M_6	M_7
0	0	0	$x + y + z$	M_0	0	1	1	1	1	1	1	1
0	0	1	$x + y + \bar{z}$	M_1	1	0	1	1	1	1	1	1
0	1	0	$x + \bar{y} + z$	M_2	1	1	0	1	1	1	1	1
0	1	1	$x + \bar{y} + \bar{z}$	M_3	1	1	1	0	1	1	1	1
1	0	0	$\bar{x} + y + z$	M_4	1	1	1	1	0	1	1	1
1	0	1	$\bar{x} + y + \bar{z}$	M_5	1	1	1	1	1	0	1	1
1	1	0	$\bar{x} + \bar{y} + z$	M_6	1	1	1	1	1	1	0	1
1	1	1	$\bar{x} + \bar{y} + \bar{z}$	M_7	1	1	1	1	1	1	1	0

More examples of two-level logic

$$f(a, b, c, d) = \sum m(1, 4, 8, 10, 13, 15)$$

$$f(w, x, y, z) = \prod M(5, 13, 14)$$

$$f(u, v) = u + \bar{u}\bar{v}$$


Logic minimization motivation

- K-maps work well for small problems
 - Too error-prone for large problems
 - Don't ensure optimal prime implicant selection
- Quine-McCluskey optimal and can be run by a computer
 - Too slow on large problems
- Some advanced heuristics usually get good results fast on large problems
- Want to learn how these work and how to use them?
- Take Advanced Digital Logic Design

Boolean function minimization


- Algebraic simplification
 - Not systematic
 - How do you know when optimal solution has been reached?
- Optimal algorithm, e.g., Quine-McCluskey
 - Only fast enough for small problems
 - Understanding these is foundation for understanding more advanced methods
- Not necessarily optimal heuristics
 - Fast enough to handle large problems

Karnaugh maps

 


Sum of products (SOP) - KMap

 Equivalent way of expressing the same function:



Implicants

For now, treat \times as a "wildcard"

 

Prime implicants are not covered by other implicants Essential prime implicants uniquely cover minterms

Karnaugh maps (K-maps)

- Fundamental attribute is adjacency
- Useful for logic synthesis
- Helps logic function visualization
- General Idea: Circle groups of output values (typically 1's)
- Result: Circled terms correspond to minimized product terms

Sum of products (SOP) - Truth table

a	b	f
0	0	1
0	1	0
1	0	0
1	1	1

$$f = (\bar{a}\bar{b}) + (ab)$$

Some definitions

- implicant* - a product term (or sum term) which covers/includes one or more minterms (or maxterms)
- prime implicant* - implicant that cannot be covered by a more general implicant (i.e. one with fewer literals)
- essential prime implicants* - cover an output of the function that no other prime implicant (or sum thereof) is able to cover

K-map example

- Minimize $f(a, b, c, d) = \sum(1, 3, 8, 9, 10, 11, 13)$
- $f(a, b, c, d) = a\bar{b} + \bar{b}d + a\bar{c}d$

K-map simplification technique

For all minterms

- Find maximal groupings of 1's and X's adjacent to that minterm.
- Remember to consider top/bottom row, left/right column, and corner adjacencies.
- These are the prime implicants.

28

R. Dick

Introduction to Computer Engineering – EECS 203

K-map simplification technique

- If there remain 1's not covered by essential prime implicants,
- Then select the smallest number of prime implicants that cover the remaining 1's.
- This can be difficult for complicated functions.
- Will present an algorithm for this in a future lecture.

30

R. Dick

Introduction to Computer Engineering – EECS 203

POS K-map techniques

- Direct reading by covering zeros and inverting variables

Or

- Invert function
- Do SOP
- Invert again
- Apply De Morgan's laws

32

R. Dick

Introduction to Computer Engineering – EECS 203

SOP from Karnaugh map

	00	01	11	10
00	1	1	0	1
01	0	0	0	0
11	0	1	1	1
10	1	1	0	1

34

R. Dick

Introduction to Computer Engineering – EECS 203

K-map simplification technique

- Revisit the 1's elements in the K-map.
- If covered by single prime implicant, the prime is essential, and participates in final cover.
- The 1's it covers do not need to be revisited.

29

R. Dick

Introduction to Computer Engineering – EECS 203

Product of sums (POS)

	0	1
0	1	0
1	0	1

$$(\bar{a} + b) \cdot (a + \bar{b})$$

31

R. Dick

Introduction to Computer Engineering – EECS 203

POS K-map example

- Minimize $f(a, b, c) = \prod(2, 4, 5, 6)$
- $f(a, b, c) = (\bar{b} + c)(\bar{a} + b)$

33

R. Dick

Introduction to Computer Engineering – EECS 203

Six-variable K-map example


$$z(a, b, c, d, e, f) = \sum(2, 8, 10, 18, 24, 26, 34, 37, 42, 45, 50, 53, 58, 61)$$

35

R. Dick

Introduction to Computer Engineering – EECS 203

Six-variable K-map example

 


Six-variable K-map example

$$z(a, b, c, d, e, f) = \bar{d}e\bar{f} + ad\bar{e}f + \bar{a}C\bar{d}\bar{f}$$

DON'T CARE logic

- All specified Boolean values are 0 or 1
- However, during design some values may be unspecified
 - Don't care values (×)
- ×s allow circuit optimization, i.e.,
 - Incompletely specified functions allow optimization

Satisfiability DON'T CARES

 


- Input can never occur
- This can happen within a circuit
- Some modules will not be capable of producing certain outputs

Don't care K-map example

- Minimize $f(w, x, y, z) = \sum(1, 3, 8, 9, 10, 11, 13) + d(5, 7, 15)$
- $f(w, x, y, z) = w\bar{x} + z$


DON'T CARE values

 

Instead, leave these values undefined (×)


- Also called DON'T CARE values
- Allows any function implementing the specified values to be used
- E.g., could use $(\bar{a}\bar{b}) + (ab)$
- However, best to use simpler 1

Observability DON'T CARES

 

Output will be ignored for certain inputs

Two-level logic is necessary

 

Some Boolean functions can not be represented with one logic level
 $(\bar{a}\bar{b}) + (ab)$

Two-level logic is sufficient

$f(a,b)$		b	
		0	1
a	0	1	0
	1	0	1

- All Boolean functions can be represented with two logic levels
- Given k variables, 2^k minterm functions exist
- Select arbitrary union of minterms

44

R. Dick

Introduction to Computer Engineering – EECS 203

Two-level sometimes impractical

$f(a,b,c,d)$		cd			
		00	01	11	10
ab	00	0	1	0	1
	01	1	0	1	0
	11	0	1	0	1
	10	1	0	1	0

Consider a 4-term XOR (parity) gate: $a \oplus b \oplus c \oplus d$
 $(\bar{a}\bar{b}\bar{c}d) + (\bar{a}\bar{b}c\bar{d}) + (\bar{a}b\bar{c}\bar{d}) + (\bar{a}bcd) + (ab\bar{c}d) + (abc\bar{d}) + (a\bar{b}\bar{c}\bar{d}) + (a\bar{b}cd)$

46

R. Dick

Introduction to Computer Engineering – EECS 203

Two-level weakness

Two-level representations also have other weaknesses

- Conversion from SOP to POS is difficult
 - Inverting functions is difficult
 - -ing two SOPs or +ing two POSs is difficult
- Neither general POS or SOP are canonical
 - Equivalence checking difficult
- POS satisfiability $\in \mathcal{NP}$ -complete

48

R. Dick

Introduction to Computer Engineering – EECS 203

Two-level well-understood

- As we will see later, optimal minimization techniques known for two-level
- However, optimal two-level solution may not be optimal solution
 - Sometimes a suboptimal solution to the right problem is better than the optimal solution to the wrong problem

45

R. Dick

Introduction to Computer Engineering – EECS 203

Two-level weakness

- Two-level representation is exponential
- However, it's a simple concept
 - Is $\sum_i^n x_i$ odd?
- Problem with representation, not function

47

R. Dick

Introduction to Computer Engineering – EECS 203

Reading assignment

- M. Morris Mano and Charles R. Kime. *Logic and Computer Design Fundamentals*. Prentice-Hall, NJ, fourth edition, 2008
- Section 2.6
- Also read TTL reference, Don Lancaster. *TTL Cookbook*. Howard W. Sams & Co., Inc., 1974, as needed

50

R. Dick

Introduction to Computer Engineering – EECS 203