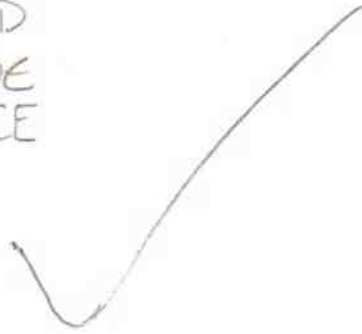


Homework 3

73

1a) Cube | Kernel

B	$AC + CD + AD$
C	$AB + BD + DE$
D	$BC + AB + CE$
AB	$C + D$
BC	$A + D$
BD	$C + A$
CD	$B + E$




b) initial # of literals = 12

$$L = AB(C+D) + BCD + CDE$$

$$L = AB(C+D) + CD(B+E)$$

final # of literals = 8

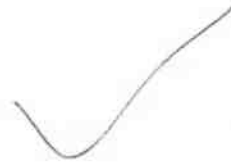

2a) $F = A\bar{B}\bar{C} + \bar{A}\bar{C} + \bar{A}B$

$$= A\bar{B}\bar{C} + \bar{A}\bar{C}(1+B) + \bar{A}B$$

$$= A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{C} + \bar{A}B$$


$$= (A+\bar{A})\bar{B}\bar{C} + \bar{A}\bar{C}(B+\bar{B}) + \bar{A}B$$

$$= \bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}B$$

$$= \bar{B}\bar{C}(1+\bar{A}) + \bar{A}B(1+\bar{C})$$

$$= \bar{B}\bar{C} + \bar{A}B$$
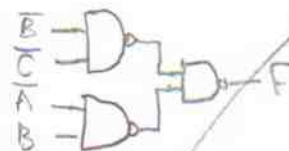
$$= \overline{(\bar{B}\bar{C})}(\bar{A}B)$$



6 PMOS
6 NMOS



b) $F = \bar{B}\bar{C} + \bar{A}B$

$$= \bar{B}\bar{C}(1+\bar{A}) + \bar{A}B(1+\bar{C})$$

$$= \bar{B}\bar{C} + \bar{A}B + \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C}$$


$$= \bar{B}\bar{C} + \bar{A}B + \bar{A}\bar{C}(B+\bar{B})$$

$$= \bar{B}\bar{C} + \bar{A}B + \bar{A}\bar{C} + B\bar{B}$$

$$= \bar{C}(\bar{A}+\bar{B}) + B(\bar{A}+\bar{B})$$

$$= \overline{(B+\bar{C})}(\bar{A}+\bar{B})$$
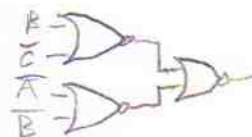
$$= \overline{(B+\bar{C})} + (\bar{A}+\bar{B})$$



6 PMOS
6 NMOS




2. $F(A,B,C) = A\bar{B}\bar{C} + \bar{A}\bar{C} + \bar{A}B$

(a)

		BC			
		00	01	11	10
A	0	1		1	1
	1	1			

$F = \bar{B}\bar{C} + \bar{A}B$

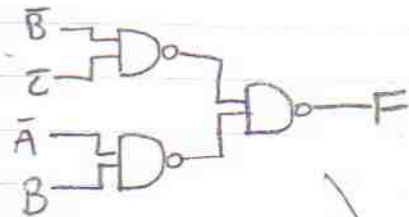$F = \overline{\overline{\bar{B}\bar{C} + \bar{A}B}}$
 $= \overline{(\bar{B}\bar{C})(\bar{A}B)}$




6 PMOS (2 per NAND)
 6 NMOS (2 per NAND)

(b)

		BC			
		00	01	11	10
A	0		1		
	1		1	1	1

$\bar{F} = \bar{B}\bar{C} + AB$

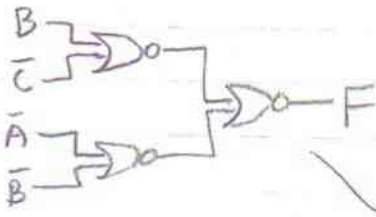$F = \overline{\bar{B}\bar{C} + AB}$
 $= \overline{(B+\bar{C})(\bar{A}+B)}$




6 PMOS (2 per NOR)
 6 NMOS (2 per NOR)

(c)


A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

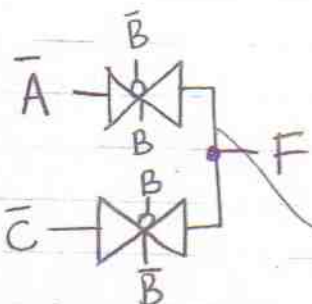$1 > \bar{C}$
 $1 > \bar{A}$
 $1 > \bar{C}$
 $1 > \bar{A}$





2 PMOS (1 per TG)
 2 NMOS (1 per TG)

3. $F(A,B,C,D) = \bar{A}BC + AD + AC$

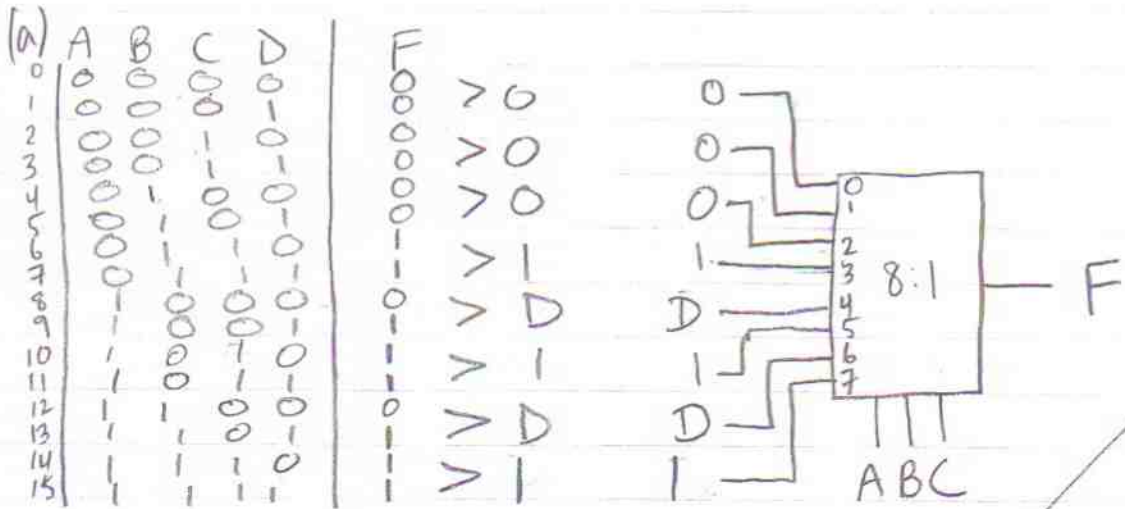

(b)

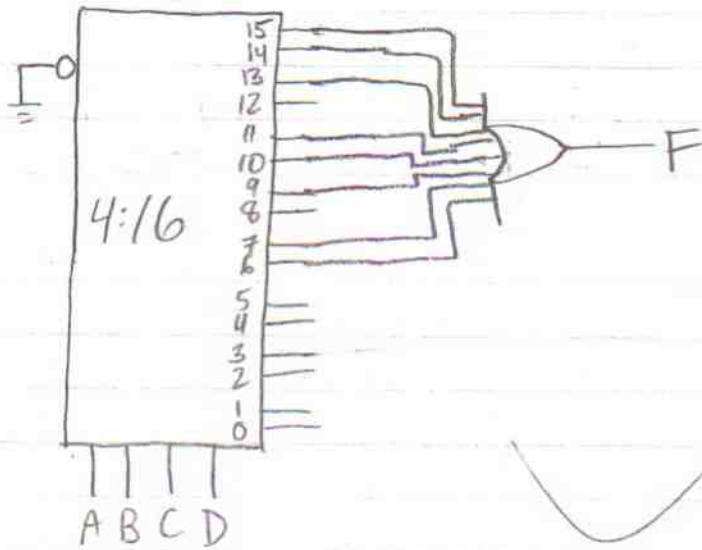

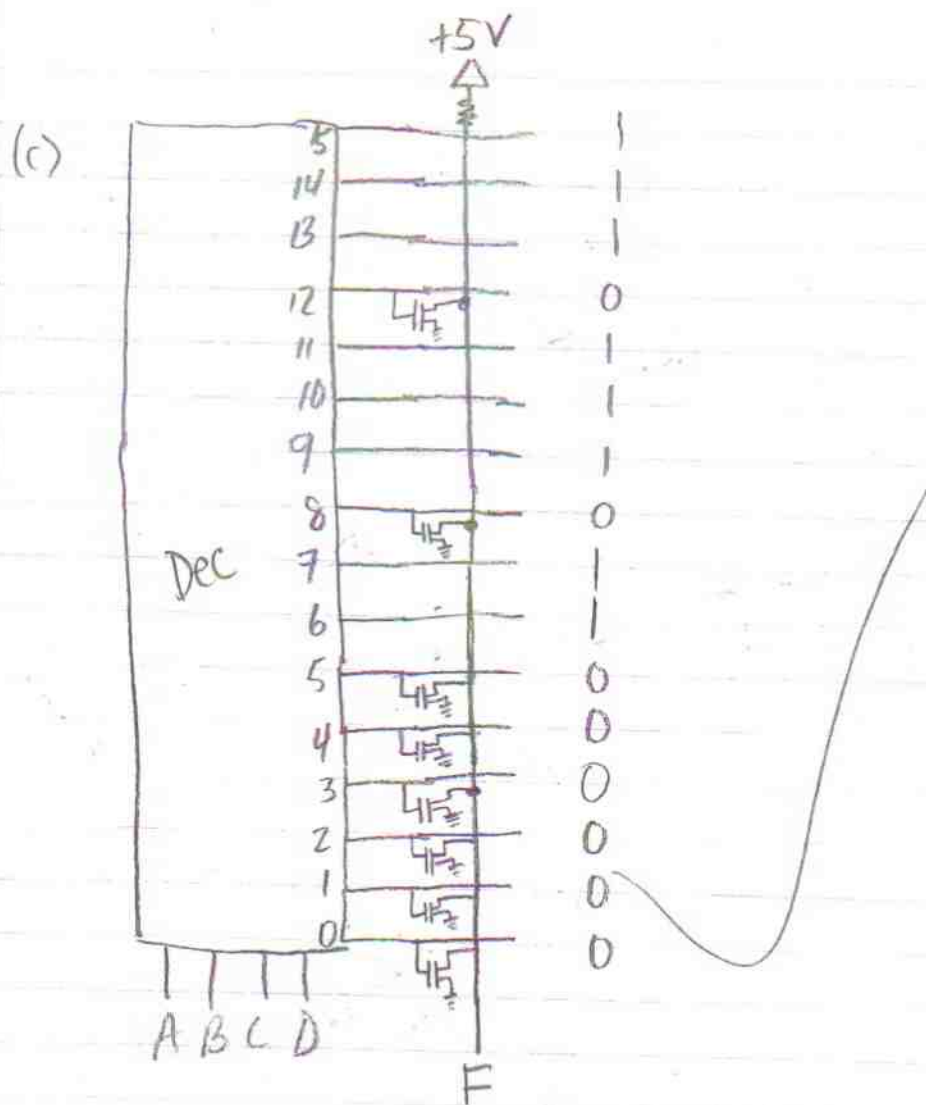

4. (a) $G = AC + \bar{A}DE + BC + BDE$ 10 literals
 kernels: A, B, C, AD, AE, BD, BE, DE

$$G = AC + BC + (A+B)DE$$


$$G = (A+B)C + (A+B)DE$$

kernels: (A+B)

$$G = (A+B)(C+DE)$$

5 literals

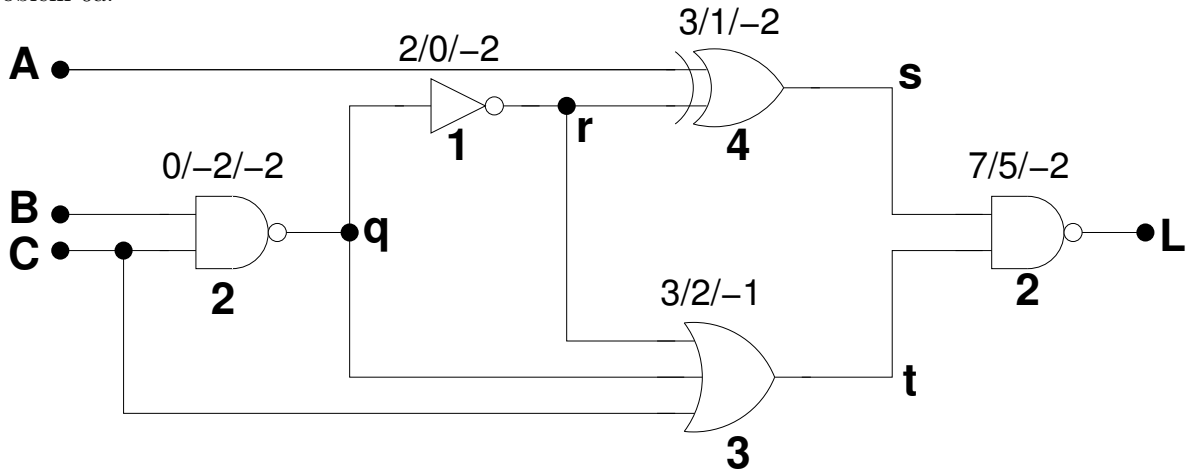- Problem 4: See slides for further examples of kernel extraction.
- Problem 5: A *graph* is composed of a set of vertices and edges. Each edge is connected to exactly two vertices. The edges in a *directed graph* are asymmetric: each has a source and destination (indicated by an arrow). A *directed acyclic graph* contains no cycles, i.e., it is impossible to start from any vertex and, following edges in the forward direction only, revisit the same vertex again. A *tree* is a directed acyclic graph containing no reconverging paths.
- Problem 6a:




Key: EST/LST/slack

The circuit does not meet its timing constraints.

- Problem 6b:

A	B	C	L
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

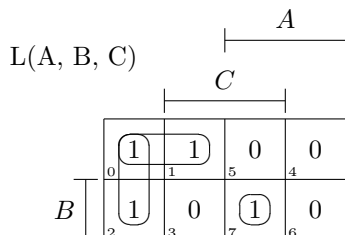

$$L(A, B, C) = \overline{A}\overline{B} + \overline{A}\overline{C} + ABC \quad (1)$$

$$= \overline{A}(\overline{B} + \overline{C}) + A(BC) \quad (2)$$

$$= \overline{A}(\overline{BC}) + A(BC) \quad (3)$$

$$= A \oplus \overline{BC} \quad (4)$$

$$= \text{XOR}(A, \text{NAND}(BC)) \quad (5)$$

Total delay = 6 (NAND2 followed by XOR2).

- Problem 6c:

