

# EECS 312 Discussion 11

11/15



Shengshuo Lu  
([luss@umich.edu](mailto:luss@umich.edu))

# Overview


- Reminder
  - Hw 4: Due Nov 20
- Sequential Logic

# Sequential Logic

# Flip-flop (Basics)

  

# Flip-flop


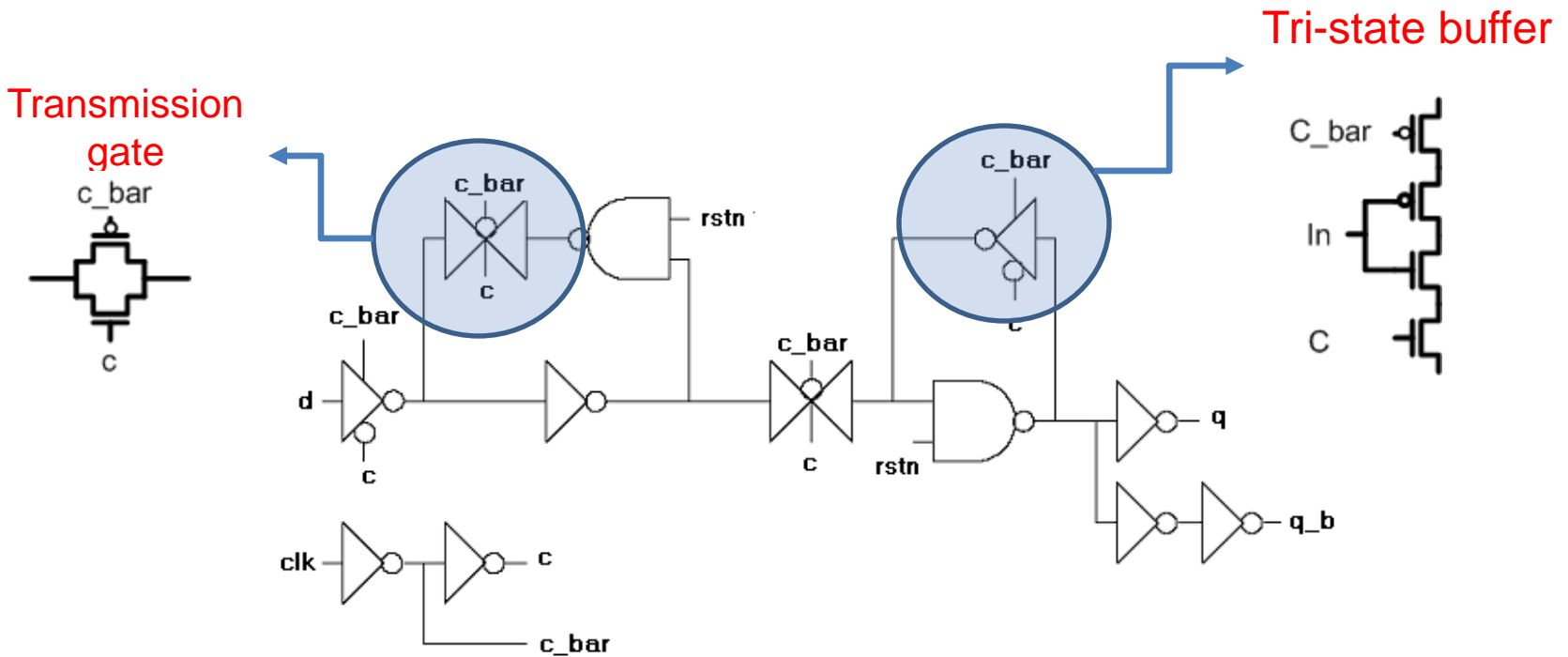


- Flip Flop with Asynchronous Reset

# Flip-flop
  
## How it works


- Divided flip flop into 2 latches (master and slave)
- When master is transparent, slave holds.
- When master holds, slave is transparent
- Capture data at the rising edge of clock


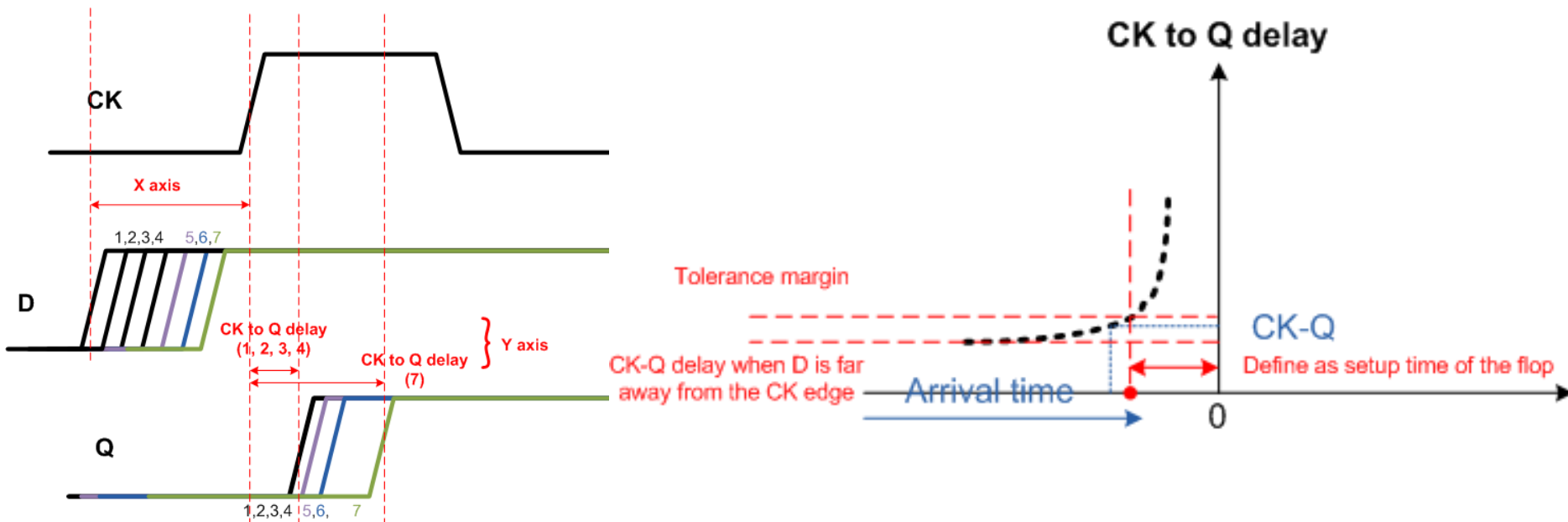
# Flip-flop (continued)

- Setup Time

- As D approaches to CK edge, C-Q delay goes up





When D arrives after the setup time point, we call it setup time violation

Setup-Time : Point at which CLK-Q delay rises 5% beyond nominal
  
# Flip-flop (continued)


- Hold Time

- Input should be stable for a period of time after the clk edge







# Synchronous Timing

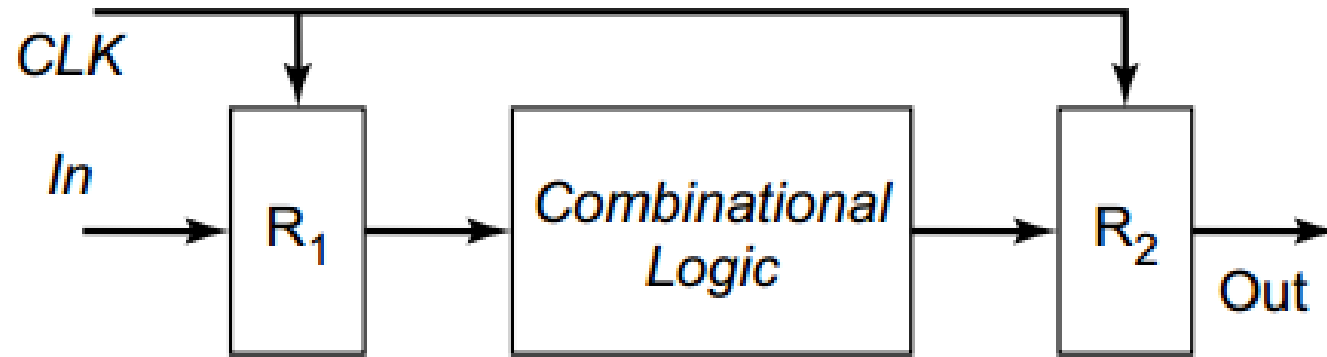

# Timing Metrics

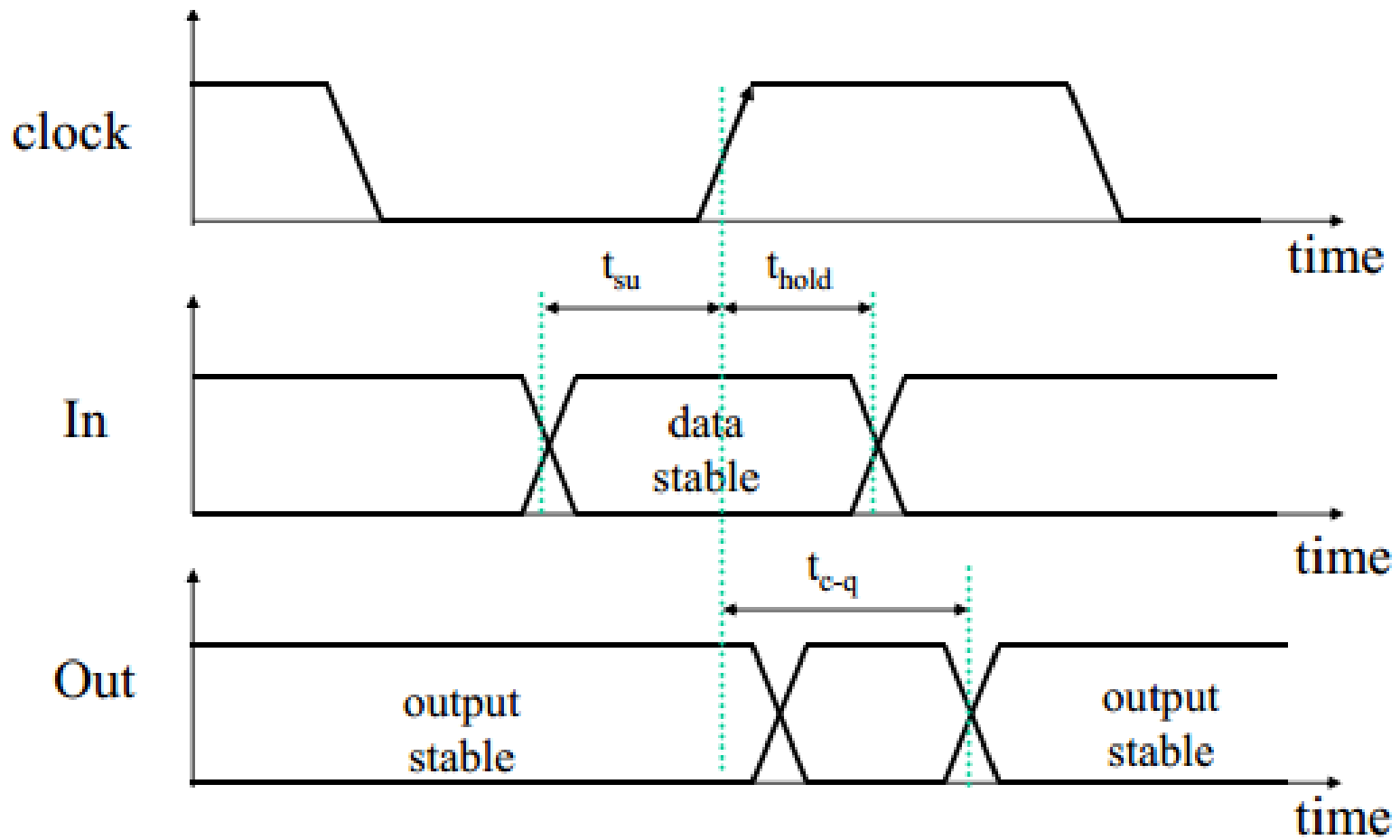

# Synchronous Timing

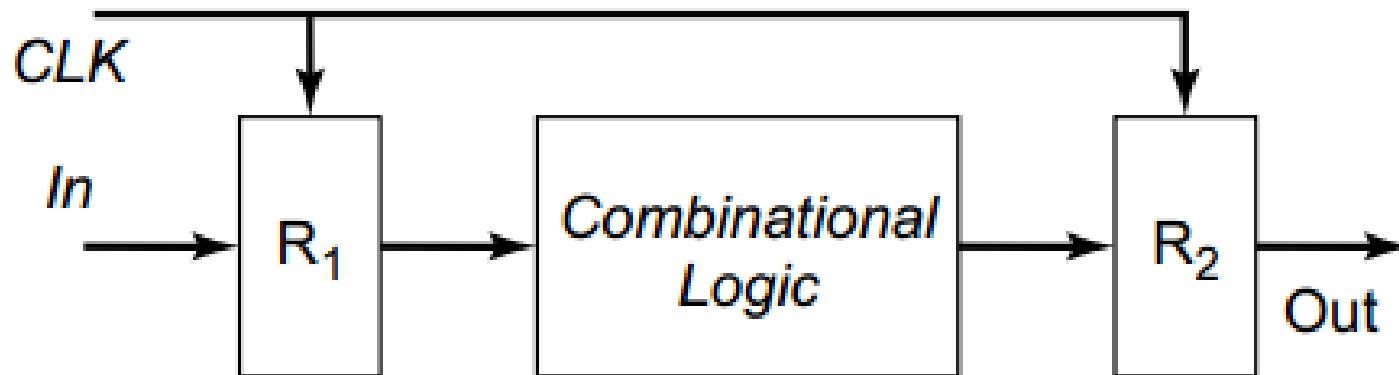

$$T_{c-q} + t_{plogic,min} \geq t_{hold}$$

$$T \geq t_{c-q} + t_{plogic,max} + t_{su}$$