 


Pass-Transistor Logic and Dynamic Logic


1

PTL AND Gate




2

NMOS-Only Logic

 

3

NMOS-only Switch

 


V_B does not pull up to 2.5V, but $2.5\text{V} - V_T$

Threshold voltage loss causes
static power consumption

NMOS has higher threshold than PMOS (body effect)

4

 
NMOS Only Logic: Level Restoring Transistor



- Advantage: Full Swing
- Restorer adds capacitance, takes away pull down current at X
- Ratio problem

5


Restorer Sizing

 

- Upper limit on restorer size
- Pass-transistor pull-down can have several transistors in stack

6


 
Solution 2: Single Transistor Pass Gate with $V_T=0$



WATCH OUT FOR LEAKAGE CURRENTS


7

Solution 3: Transmission Gate

  


8

Resistance of Transmission Gate

 

9

Transmission Gate XOR

 


10

Dynamic CMOS

- In **static** circuits at every point in time (except when switching) the output is connected to either GND or V_{DD} via a low resistance path.
 - fan-in of n requires $2n$ (n N-type + n P-type) devices
- **Dynamic** circuits rely on the temporary storage of signal values on the capacitance of high impedance nodes.
 - requires on $n + 2$ ($n+1$ N-type + 1 P-type) transistors


11

Dynamic Gate

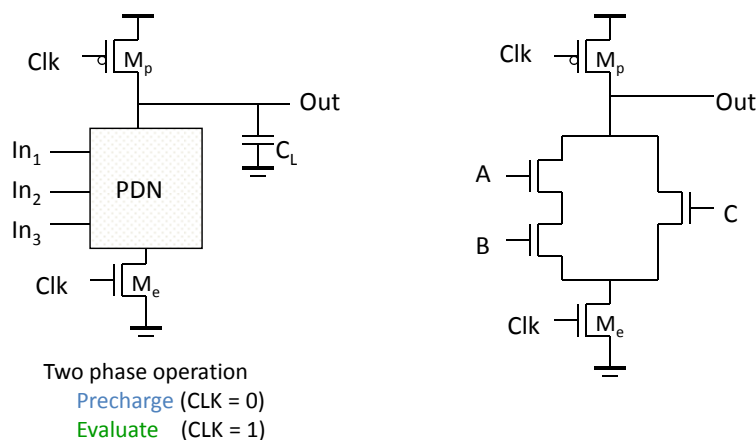


12

Dynamic Gate

 

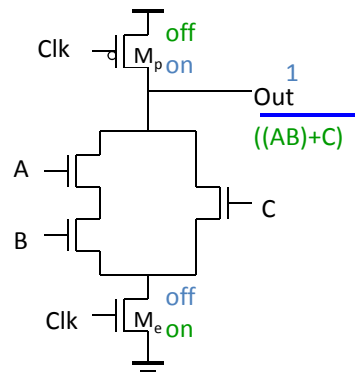Two phase operation
 Precharge (Clk = 0)
 Evaluate (Clk = 1)



13

Conditions on Output

- Once the output of a dynamic gate is discharged, it cannot be charged again until the next precharge operation.
- Inputs to the gate can make **at most** one transition during evaluation.
- Output can be in the high impedance state during and after evaluation (PDN off), state is stored on C_L

14

Properties of Dynamic Gates

- Logic function is implemented by the PDN only
 - number of transistors is $N + 2$ (versus $2N$ for static complementary CMOS)
- Full swing outputs ($V_{OL} = \text{GND}$ and $V_{OH} = V_{DD}$)
- Non-ratioed - sizing of the devices does not affect the logic levels
- Faster switching speeds
 - reduced load capacitance due to lower input capacitance (C_{in})
 - reduced load capacitance due to smaller output loading (C_{out})
 - no I_{sc} , so all the current provided by PDN goes into discharging C_L


15

Properties of Dynamic Gates

- Overall power dissipation usually higher than static CMOS
 - no static current path ever exists between V_{DD} and GND (including P_{sc})
 - no glitching
 - higher transition probabilities
 - extra load on Clk
- PDN starts to work as soon as the input signals exceed V_{Tn} , so V_M , V_{IH} and V_{IL} equal to V_{Tn}
 - low noise margin (NM_L)
- Needs a precharge/evaluate clock

16

 
Issues in Dynamic Design 1: Charge Leakage



Dominant component is subthreshold current

17

Solution to Charge Leakage

 

Same approach as level restorer for pass-transistor logic

18