
 
 


Digital Integrated Circuits – EECS 312

<http://robertdick.org/eecs312/>

Teacher: Robert Dick
Office: 2417-E EECS
Email: dickrp@umich.edu
Phone: 734-763-3329
Cellphone: 847-530-1824

 GSI: Shengshou Lu
Office: 2725 BBB
Email: luss@umich.edu



Announcements

- Logical effort.
- Homework 3, problem 9 will be moved to Homework 4.
- Review DeMorgan's Laws and gate design.

Examples

- $f(a) = a$.
- $f(a) = \bar{a}$
- $f(a, b) = a\bar{b}$
- $f(a, b) = ab$ (Check Figure 6-33 in J. Rabaey, A. Chandrakasan, and B. Nikolic. *Digital Integrated Circuits: A Design Perspective*. Prentice-Hall, second edition, 2003!)
- $f(a, b, c) = ab + \bar{b}c$ (try both ways).

Derive and explain.


Lecture plan

1. Non-idealities
2. DCVSL
3. Dynamic CMOS
4. Charge sharing
5. Homework

Miller effect

- If V_D switches in the opposite direction of V_G , the effect of C_{GD} is doubled.
- Consider an inverter.
- Model by using a $2C_{GD}$ capacitor to ground.

Stack effect

 


- Each series transistor drops the voltage seen by the next transistor.
- $V_T = V_{T0} + \gamma \left(\sqrt{|-2\phi_F + V_{SB}|} - \sqrt{|2\phi_F|} \right)$
- $V_{Tn2} = V_{Tn0} + \gamma \left(\sqrt{|2\phi_F + V_{int}|} - \sqrt{|2\phi_F|} \right)$

Dynamic hazards

- Potential for two or more spurious transitions before intended transition
- Results from uneven path delays in some multi-level circuits



Dynamic hazards

 


Eliminating dynamic hazards

- Some approaches allow preservation of multi-level structure
 - Quite complicated to apply
- Simpler solution – Convert to two-level implementation

Static hazards


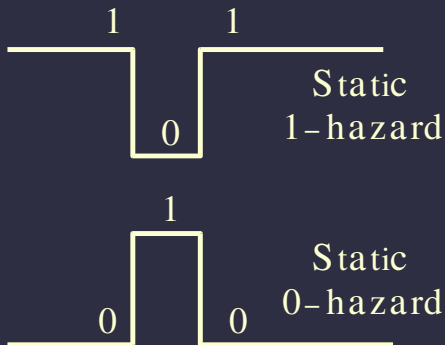
- Still have static hazards
- Potential for transient change of output to incorrect value



Problems with glitches

- These transitions result in incorrect output values at some times
- Also result in uselessly charging and discharging wire and gate capacitances through wire, gate, and channel resistances
 - Increase power consumption

Glitches increase power consumption

  

Detecting hazards

- The observable effect of a hazard is a glitch
 - A circuit that might exhibit a glitch has a hazard
- Whether or not a hazard is observed as a glitch depends on relative gate delays
- Relative gate delays change depending on a number of factors – Conditions during fabrication, temperature, age, etc.
- Best to use abstract reasoning to determine whether hazards might be observed in practice, under some conditions

Eliminating static hazards

- Ensure that the function has a term maintaining a 0 output for all $0 \rightarrow 0$ transitions.
- Ensure that the function has a term maintaining a 1 output for all $1 \rightarrow 1$ transitions.
- There are precisely defined algorithms for this, but they build on a knowledge of logic minimization.

Where do static hazards really come from?

- Static-0: $A \bar{A}$
- Static-1: $A + \bar{A}$
- Assume SOP form has no product terms containing a variable in complemented and uncomplemented forms
 - Reasonable assumption, if true, drop product term

Where do static hazards really come from?

- Assume POS form has no sum terms containing a variable in complemented and uncomplemented forms
 - Reasonable assumption, if true, drop sum term
- Assume only one input switches at a time
- Conclusion: SOP has no 0-hazards and POS has no 1-hazards
 - In other words, if you are doing two-level design, you need not analyze the other form for hazards

Living with hazards


Sometimes hazards can be tolerated

- Combinational logic whose outputs aren't observed at all times
- Synchronous systems
- Systems without tight power consumption limits


Lecture plan

 1. Non-idealities
2. DCVSL
3. Dynamic CMOS
4. Charge sharing
5. Homework


Differential cascode voltage switch logic



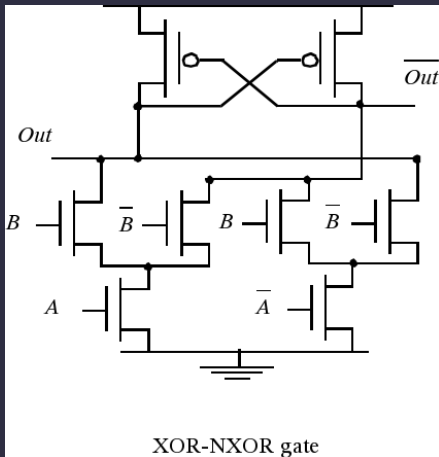
Differential cascode voltage switch logic example



 
Differential cascode voltage switch logic response




NMOS-only wired and

 


Level restoration

 

Restorer sizing

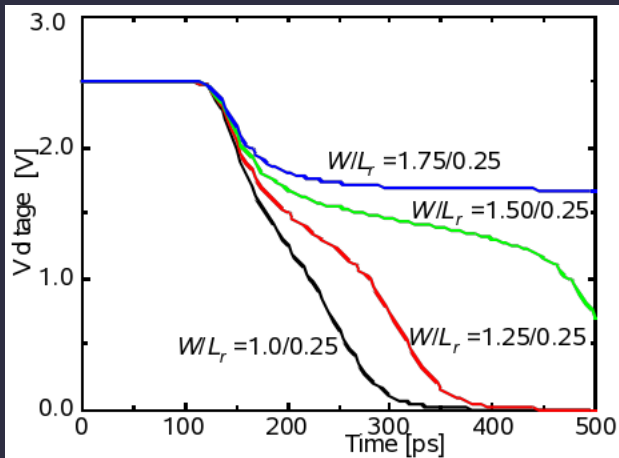

 Depletion mode $V_T = 0\text{ V}$ pass transistor



Consider leakage.


Lecture plan

1. Non-idealities
2. DCVSL
3. Dynamic CMOS
4. Charge sharing
5. Homework

Static vs. dynamic logic


- Static logic relies only on steady-state behavior of system. Eventually the output converges to a correct result.
- Dynamic logic relies on transient behavior and is sensitive to timing. Reliable design is generally trickier. Why use it?
- Static logic requires $(k_P + k_N)$ transistors for k -input gate.
- Dynamic logic requires $k_N + 2$ transistors for k -input gate.

Dynamic logic

 

Two-phase operation.

Dynamic logic example

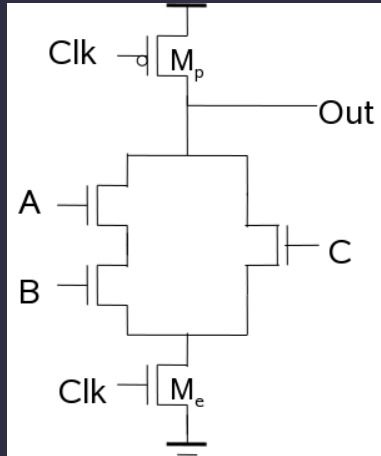

Dynamic logic operating principles I

- 1 Can only discharge output node once per clock period.
- 2 Inputs must make only one transition during evaluation.
- 3 Output can be in the high impedance state during and after evaluation.
- 4 Logic function is implemented by the pull-down network only.
- 5 Requires only $k_N + 2$ transistors.
- 6 Full swing outputs.
- 7 Non-ratioed - sizing of the devices does not affect the logic levels.
- 8 Reduced load capacitance due to lower input capacitance.
- 9 Reduced load capacitance due to smaller output loading. no I_{sc} , so all the current provided by PDN goes into discharging CL.

Dynamic logic operating principles II

- ⑩ Power consumption usually higher than static CMOS.
 - Good: No static current.
 - Good: No glitching.
 - Bad: Higher transition probabilities.
 - Bad: More load on clock distribution network.
- ⑪ $V_M = V_{IH} = V_{IL} = V_{TN}$ so noise margin is low.
- ⑫ Needs precharge and evaluation cycle.

Upcoming topics

- Example problems on recently covered material.
- Latches and flip-flops.

Review


- What are dynamic hazards?
- What are static hazards?
- What problems do hazards cause?
- What is the root cause of static hazards?
- Let's implement a function using DCVSL.

Derive and explain.


Lecture plan

1. Non-idealities
2. DCVSL
3. Dynamic CMOS
4. Charge sharing
5. Homework


Dynamic logic charge leakage

 

 
Dynamic logic charge leakage timing diagram




Leakage prevention

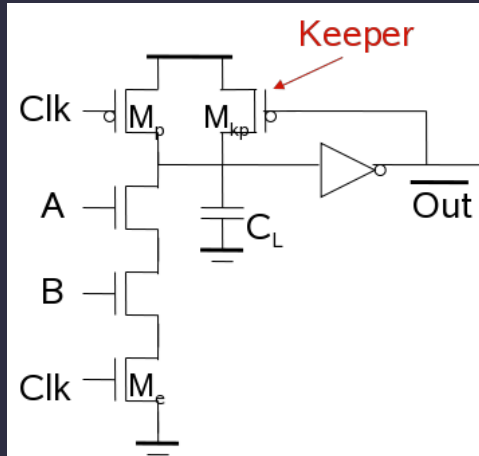

Charge sharing

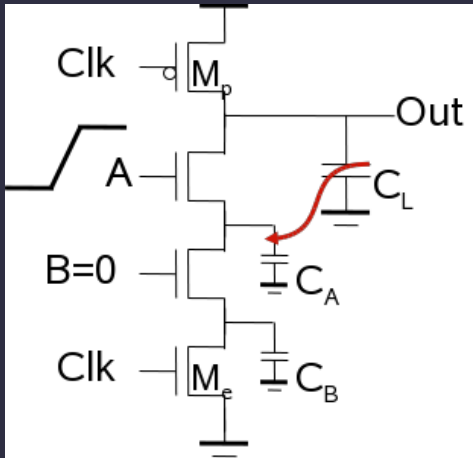

Charge sharing model

 


- 1 Determine condition by setting $\Delta V_{out} = V_{Tn}$.
- 2 This yields $\frac{C_a}{C_L} = \frac{V_{Tn}}{V_{DD} - V_{Tn}}$.

Charge sharing equations


$$\Delta V_{out} = \begin{cases} V_{out}^{(final)} + V_{DD} = -C_a/C_L \left(V_{DD} - V_{Tn}^{(V_X)} \right) & \text{if } \Delta V_{out} < V_{Tn} \\ -V_{DD} \frac{C_a}{C_a + C_L} & \text{if } \Delta V_{out} > V_{Tn} \end{cases}$$

Note: The book has a sign error when deriving the boundary point.

Preventing charge sharing problems

 

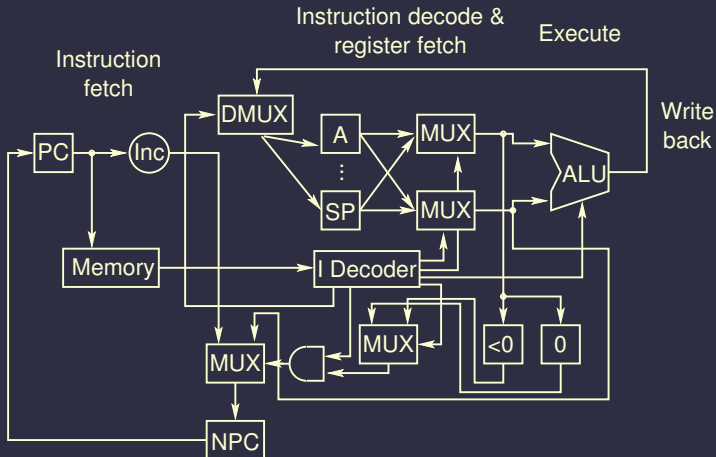Transition from combinational to sequential circuits



Upcoming topics

- Sense amplifiers.
- A more formal approach to gate sizing.

Lecture plan

1. Non-idealities
2. DCVSL
3. Dynamic CMOS
4. Charge sharing
5. Homework

Homework assignment

- 31 October: Read Sections 6.3 and 7.1 in J. Rabaey, A. Chandrakasan, and B. Nikolic. *Digital Integrated Circuits: A Design Perspective*. Prentice-Hall, second edition, 2003.
- 7 November: Project 4.