
 
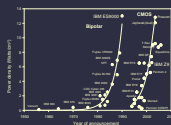
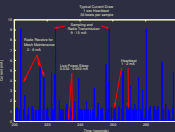


# Digital Integrated Circuits – EECS 312

<http://ziyang.eecs.umich.edu/~dickrp/eecs312/>

Teacher: Robert Dick  
Office: 2417-G EECS  
Email: [dickrp@eecs.umich.edu](mailto:dickrp@eecs.umich.edu)  
Phone: 734-763-3329  
Cellphone: 847-530-1824

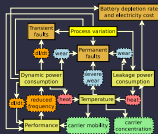GSI: Myung-Chul Kim  
Email: [mckima@umich.edu](mailto:mckima@umich.edu)



# Review

- How can the optimal number of inverters in a load-driving chain be determined?
- How can the optimal size of each inverter in the chain be decided?
- How do determine optimal sizes of logic gates in arbitrary structures?
- Do example problem.

Derive and explain.

# Review

- How can the optimal number of inverters in a load-driving chain be determined?
- How can the optimal size of each inverter in the chain be decided?
- How do determine optimal sizes of logic gates in arbitrary structures?
  - May cover this near end of course.
- Do example problem.

Derive and explain.

## Lab 3

- Transistor sizing in logic gates.
- Due 12:00 midnight. Fine to establish completion time by emailing report, but please hand in hardcopy by Thursday.

Derive and explain.

## Speakers and topics

- 4 November: Katherine, Olga, and Matt. Atomic layer deposition.
- 11 November: Ike and Dan. ALU design alternatives.
- 16 November: Michael, Heesung, and Jiayi. Impact of materials on devices and circuits.
- Haishan and Guanyu. Optical interconnect.
- Tyler and Megan. Subthreshold circuit applications.
- Sui Yu, Zhenghong and Wang Yi. FinFETs.
- Bo Zhu, Terence, and Baishun. Resonant tunneling devices.
- Shaobing and Haoyu. Circuit Elements Improvement for Wireless Sensor Network.
- Austin: Memristors.

# Lecture plan

1. Impact of input voltage function on energy consumption
2. Interconnect modeling
3. Homework

# Power consumption in synchronous CMOS

$$P = P_{SWITCH} + P_{SHORT} + P_{LEAK}$$

$$P_{SWITCH} = C \cdot V_{DD}^2 \cdot f \cdot A$$

$$\dagger P_{SHORT} = \frac{b}{12} (V_{DD} - 2 \cdot V_T)^3 \cdot f \cdot A \cdot t$$

$$P_{LEAK} = V_{DD} \cdot (I_{SUB} + I_{GATE} + I_{JUNCTION} + I_{GIDL})$$

$C$  : total switched capacitance

$V_{DD}$  : high voltage

$f$  : switching frequency

$A$  : switching activity

$b$  : MOS transistor gain

$V_T$  : threshold voltage

$t$  : rise/fall time of inputs

$\dagger P_{SHORT}$  usually  $\leq 10\%$  of  $P_{SWITCH}$

Smaller as  $V_{DD} \rightarrow V_T$

$A < 0.5$  for combinational nodes, 1 for clocked nodes.

# Reasons for power consumption

- Dynamic
  - Charging and discharging RC loads.
  - $E_{dyn} = C_L V_{DD}^2$ .
  - $P_{dyn} = C_L V_{DD}^2 f$ .
  - But  $f \propto V_{DD}$ .
  - So  $P_{dyn} = C_L V_{DD}^3$ .
- Static
  - Sub-threshold leakage.
  - Gate leakage.
- Short-circuit: Pull-up and pull-down networks briefly both on.

## Fixed voltage charging

$$E_R^{step} = \int_{t=0}^{\infty} V_R(t) I_R(t) dt$$

# Fixed voltage charging

$$E_R^{step} = \int_{t=0}^{\infty} V_R(t) I_R(t) dt$$

$$E_R^{step} = \int_{t=0}^{\infty} V_R(t) \frac{V_R(t)}{R} dt$$

$$E_R^{step} = \int_{t=0}^{\infty} V_{DD} e^{-t/RC} \frac{V_{DD} e^{-t/RC}}{R} dt$$

$$E_R^{step} = \frac{V_{DD}^2}{R} \int_{t=0}^{\infty} e^{-2t/R} dt$$

$$E_R^{step} = \frac{V_{DD}^2}{R} \left( -\frac{RC}{2} \right) \left( e^{-2t/RC} \right)_{t=0}^{\infty}$$

$$E_R^{step} = \frac{-V_{DD}^2 C}{2} (0 - 1)$$

$$E_R^{step} = \frac{V_{DD}^2 C}{2}$$

## Fixed current charging I

$$E_R^{ramp} = \int_{t=0}^{\infty} V_R(t) I_R(t) dt$$

Let  $T$  be the voltage ramp duration,  $I_R$  is fixed.  $V_R$  is fixed.

## Fixed current charging II

$$\Delta V = \frac{\Delta q}{C}$$

$$V_{DD} = \frac{I_R T}{C}$$

$$I_R = \frac{C V_{DD}}{T}$$

$$V_R = R I_R$$

$$E_R^{ramp} = \int_{t=0}^T V_R(t) \frac{C V_{DD}}{T} \frac{R C V_{DD}}{T} dt$$

$$E_R^{ramp} = \frac{R V_{DD}^2 C^2}{T^2} \int_{t=0}^T 1 dt$$

## Fixed current charging III

$$E_R^{ramp} = \frac{V_{DD}^2 C^2 R}{T^2} T$$

$$E_R^{ramp} = \frac{V_{DD}^2 C^2 R}{T}$$

$$E_R^{ramp} = \frac{V_{DD}^2 C}{2} \frac{2RC}{T}$$

## Break-even point

$$\begin{aligned}E_R^{step} &= E_R^{ramp} \\ \frac{V_{DD}^2 C}{2} &= \frac{V_{DD}^2 C}{2} \frac{2RC}{T} \\ 1 &= \frac{2RC}{T} \\ T &= 2RC\end{aligned}$$

- Properly controlling  $V_R(t)$ .
- Performance.
- In limit, permits reversible computation with low/no power consumption during charging and discharging.


## Charging methods summary

- $I(t)$  influences energy consumption for same change in  $V$ .
- In theory, keeping voltage differences very small can permit extremely low-power operation.
- Leakage, current control, and preserving reversibility make this challenging.


# Lecture plan

1. Impact of input voltage function on energy consumption
2. Interconnect modeling
3. Homework


# Capacitive load modeling

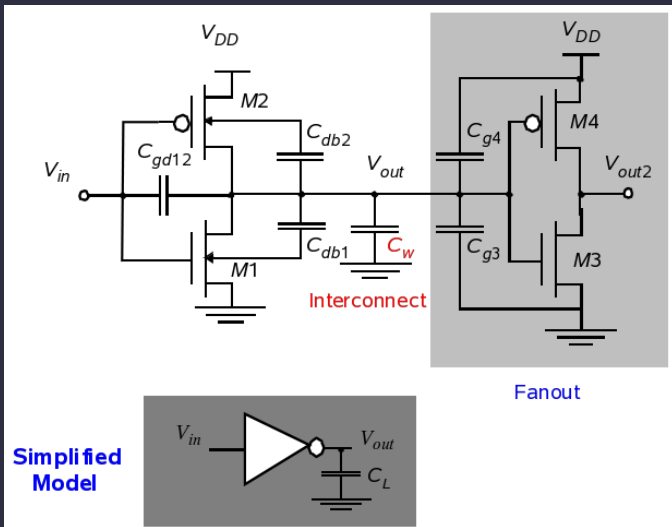

# Interconnect modeling

 

## Interconnect capacitance

 


$$C = \frac{\epsilon_{ox}}{t_{ox}} WL$$

# Permittivity ( $k$ )

| Material                       | $\epsilon$ |
|--------------------------------|------------|
| Vacuum                         | 1          |
| Aerogels                       | $\sim 1.5$ |
| Polyimides                     | 3–4        |
| SiO <sub>2</sub>               | 3.9        |
| Glass-epoxy                    | 5          |
| Si <sub>3</sub> N <sub>4</sub> | 7.5        |
| Alumina                        | 9.5        |
| Silicon                        | 11.7       |

# Fringing

 

$$C_{wire} = C_{pp} + C_{fringe} = W \frac{\epsilon_{ox}}{t_{ox}} + \frac{2\pi\epsilon_{ox}}{\log(t_{ox}/H)}$$

# Trends in interconnect design

- More metal layers.
- Higher aspect ratios.
  - More coupling.
- Smaller transistors, but similar-length global interconnect.

## Upcoming topics

- Alternative logic design styles.
- Latches and flip-flops.
- Memories.

# Lecture plan

1. Impact of input voltage function on energy consumption
2. Interconnect modeling
3. Homework

# Homework assignment

- 4 November, Thursday: Read Sections 6.2.2 and 6.2.3 in J. Rabaey, A. Chandrakasan, and B. Nikolic. *Digital Integrated Circuits: A Design Perspective*. Prentice-Hall, second edition, 2003.
- 4 November, Thursday: First short talk.
- 11 November, Thursday: Homework 3.