 


# Digital Integrated Circuits – EECS 312

<http://ziyang.eecs.umich.edu/~dickrp/eecs312/>

Teacher: Robert Dick  
Office: 2417-G EECS  
Email: dickrp@eecs.umich.edu  
Phone: 734-763-3329  
Cellphone: 847-530-1824

GSI: Myung-Chul Kim  
Email: mckima@umich.edu



## Midterm exam 2

- Requested times for midterm exam.
- 30 November or 2 December.
- Received two replies that conflict.
- Coin flip.

## Lab 4

Derive and explain.

## Examples

- $f(a) = a$ .
- $f(a) = \bar{a}$
- $f(a, b) = a\bar{b}$
- $f(a, b) = ab$  (Check Figure 6-33 in J. Rabaey, A. Chandrakasan, and B. Nikolic. *Digital Integrated Circuits: A Design Perspective*. Prentice-Hall, second edition, 2003!)
- $f(a, b, c) = ab + \bar{b}c$  (try both ways).

Derive and explain.

Non-idealities  
DCVSL  
Dynamic CMOS  
Homework

## Travel

- Where were your teacher and teaching assistant?
- International Conference on Computer-Aided Design.
- Mr. Kim won the best-paper award at this top conference.
- I gave a tutorial on integrated circuit and embedded system reliability.
- My student gave a talk on dynamic control of  $V_{DD}$  to minimize energy consumption while meeting performance requirements.
- If curious, you can out about the research on the course website, at the "Excuse for absence" link.

2 Robert Dick Digital Integrated Circuits

Non-idealities  
DCVSL  
Dynamic CMOS  
Homework

## Homework 3

- Was anybody unable to get help they needed on Homework 3?
- If so will not penalize assignments handed in by Friday.
- However, Lab 4 will be assigned today.

4 Robert Dick Digital Integrated Circuits

Non-idealities  
DCVSL  
Dynamic CMOS  
Homework

## Review

- What is the purpose of a restorer in pass transistor logic?
- What happens if the restorer MOSFET is too wide?
- What happens if the restorer MOSFET is too narrow?
- What are the advantages of dynamic logic?
- What are the disadvantages of dynamic logic?

6 Robert Dick Digital Integrated Circuits

Non-idealities  
DCVSL  
Dynamic CMOS  
Homework

## Miller effect

- If  $V_D$  switches in the opposite direction of  $V_G$ , the effect of  $C_{GD}$  is doubled.
- Consider an inverter.
- Model by using a  $2C_{GD}$  capacitor to ground.

9 Robert Dick Digital Integrated Circuits

3 Robert Dick Digital Integrated Circuits


Non-idealities  
DCVSL  
Dynamic CMOS  
Homework

5 Robert Dick Digital Integrated Circuits

Non-idealities  
DCVSL  
Dynamic CMOS  
Homework


7 Robert Dick Digital Integrated Circuits

### Stack effect

 


- Each series transistor drops the voltage seen by the next transistor.
- $V_{T1} = V_{Tn0} + \gamma \left( \sqrt{|-2\phi_F + V_{SB}|} - \sqrt{2\phi_F} \right)$
- $V_{Tn2} = V_{Tn0} + \gamma \left( \sqrt{2\phi_F + V_{int}} - \sqrt{2\phi_F} \right)$

### Dynamic hazards

 

 
### Static hazards

- Still have static hazards
- Potential for transient change of output to incorrect value




### Glitches increase power consumption

 
 
### Dynamic hazards

- Potential for two or more spurious transitions before intended transition
- Results from uneven path delays in some multi-level circuits



### Eliminating dynamic hazards

- Some approaches allow preservation of multi-level structure
  - Quite complicated to apply
- Simpler solution – Convert to two-level implementation

### Problems with glitches

- These transitions result in incorrect output values at some times
- Also result in uselessly charging and discharging wire and gate capacitances through wire, gate, and channel resistances
  - Increase power consumption

### Detecting hazards

- The observable effect of a hazard is a glitch
  - A circuit that might exhibit a glitch has a hazard
- Whether or not a hazard is observed as a glitch depends on relative gate delays
- Relative gate delays change depending on a number of factors – Conditions during fabrication, temperature, age, etc.
- Best to use abstract reasoning to determine whether hazards might be observed in practice, under some conditions

## Eliminating static hazards

- Ensure that the function has a term maintaining a 0 output for all 0→0 transitions.
- Ensure that the function has a term maintaining a 1 output for all 1→1 transitions.
- There are precisely defined algorithms for this, but they build on a knowledge of logic minimization.

18

Robert Dick

Digital Integrated Circuits

## Where do static hazards really come from?


- Assume POS form has no sum terms containing a variable in complemented and uncomplemented forms
  - Reasonable assumption, if true, drop sum term
- Assume only one input switches at a time
- Conclusion: SOP has no 0-hazards and POS has no 1-hazards
  - In other words, if you are doing two-level design, you need not analyze the other form for hazards

20

Robert Dick

Digital Integrated Circuits
 
## Differential cascode voltage switch logic




23

Robert Dick

Digital Integrated Circuits
 
## Differential cascode voltage switch logic response



25

Robert Dick

Digital Integrated Circuits

## Where do static hazards really come from?

- Static-0:  $A \bar{A}$
- Static-1:  $A + \bar{A}$
- Assume SOP form has no product terms containing a variable in complemented and uncomplemented forms
  - Reasonable assumption, if true, drop product term

19

Robert Dick

Digital Integrated Circuits

## Living with hazards

Sometimes hazards can be tolerated


- Combinational logic whose outputs aren't observed at all times
- Synchronous systems
- Systems without tight power consumption limits

21

Robert Dick

Digital Integrated Circuits
 
## Differential cascode voltage switch logic example



XOR-NXOR gate

24

Robert Dick

Digital Integrated Circuits

## Static vs. dynamic logic


- Static logic relies only on steady-state behavior of system. Eventually the output converges to a correct result.
- Dynamic logic relies on transient behavior and is sensitive to timing. Reliable design is generally trickier. Why use it?
- Static logic requires  $(k_P + k_N)$  transistors for  $k$ -input gate.
- Dynamic logic requires  $k_N + 2$  transistors for  $k$ -input gate.

27

Robert Dick

Digital Integrated Circuits

## Dynamic logic

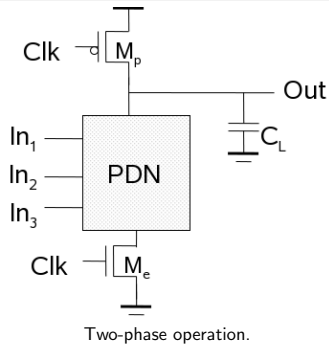

Two-phase operation.

28

Robert Dick

Digital Integrated Circuits

## Dynamic logic operating principles I

- 1 Can only discharge output node once per clock period.
- 2 Inputs must make only one transition during evaluation.
- 3 Output can be in the high impedance state during and after evaluation.
- 4 Logic function is implemented by the pull-down network only.
- 5 Requires only  $k_N + 2$  transistors.
- 6 Full swing outputs.
- 7 Non-ratioed - sizing of the devices does not affect the logic levels.
- 8 Reduced load capacitance due to lower input capacitance.
- 9 Reduced load capacitance due to smaller output loading. no Isc, so all the current provided by PDN goes into discharging CL.

30

Robert Dick

Digital Integrated Circuits

## Upcoming topics

- Example problems on recently covered material.
- Latches and flip-flops.

32


Robert Dick

Digital Integrated Circuits

## Special topic: ALU design

Daniel Clifford and Ike Anyanetu

## Dynamic logic example

 

29

Robert Dick

Digital Integrated Circuits

## Dynamic logic operating principles II

- 10 Power consumption usually higher than static CMOS.
  - Good: No static current.
  - Good: No glitching.
  - Bad: Higher transition probabilities.
  - Bad: More load on clock distribution network.
- 11  $V_M = V_{IH} = V_{IL} = V_{TN}$  so noise margin is low.
- 12 Needs precharge and evaluation cycle.

31

Robert Dick

Digital Integrated Circuits

## Homework assignment

- 11 November, Thursday: Homework 3.
- 16 November, Tuesday: Read Sections 7.1, 7.2.1–7.2.3 in J. Rabaey, A. Chandrakasan, and B. Nikolic. *Digital Integrated Circuits: A Design Perspective*. Prentice-Hall, second edition, 2003.
- 22 November, Thursday: Lab 4.

34

Robert Dick

Digital Integrated Circuits