 



Digital Integrated Circuits – EECS 312

<http://robertdick.org/eecs312/>


Teacher: Robert Dick GSI: Shengshou Lu
 Office: 2417-E EECS Office: 2725 BBB
 Email: dickrp@umich.edu Email: luss@umich.edu
 Phone: 734-763-3329
 Cellphone: 847-530-1824



NMOS inverter schematic

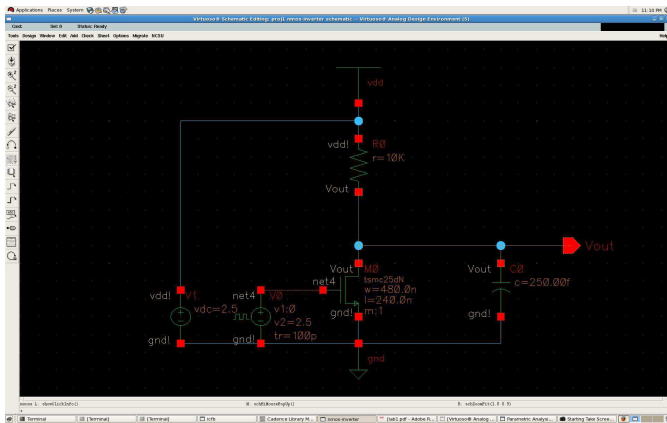

NMOS inverter simulation results

 

Lab one challenges

- Learning to use the tools (last Friday).
- Understanding the circuits used in the lab (today).
- A note on the CAD tools market.

Derive and explain.

Resistance

$$R = \rho \frac{L}{W} \quad (1)$$


$$G = \sigma \frac{W}{L} \quad (2)$$

$$G = \frac{1}{R} \quad (3)$$

$$\sigma = \frac{1}{\rho} \quad (4)$$

- Assuming fixed height.
- R : resistance.
- ρ : resistivity.
- L : length.
- W : width.
- G : conductance.

RC network

 

$$V_c = V_{final} + (V_{init} - V_{final}) e^{-\frac{t}{\tau}} \quad (5)$$

$$\tau = RC \quad (6)$$

NMOS→CMOS inverter

- How does structure change?
- What impact does transistor width have? Why different widths?
- How does response change?
- What are advantages?
- What are disadvantages?

Derive and explain.

8

Review questions and note

- What are digital systems built from?
- What gate properties are required for use in digital systems? Why?
- What have the major effects of process scaling been? What challenges does it face in the future?
- What are the physical structures and symbols of (N/P)MOSFETs? How do they work?

9

Desired and actual properties of transistors

Desired properties

- Perfect digital signal transfer.
- No parasitics.

Actual properties

- Imperfect transfer function.
 - Fortunately, has gain and capable of signal regeneration (restoration).
- Parasitic resistance and capacitance.
- Leakage.

11

Brief introduction to Boolean algebra

- The only values are 0 (or false) and 1 (or true).
- One can define operations/functions/gates.
 - Boolean values as input and output.
- A truth table enumerates output values for all input value combinations.

12

AND


a	b	$a \wedge b$
0	0	0
0	1	0
1	0	0
1	1	1



$$a \text{ AND } b = a \wedge b = a \cdot b$$

OR

a	b	$a \vee b$
0	0	0
0	1	1
1	0	1
1	1	1

 

$$a \text{ OR } b = a \vee b = a + b$$

13

14


NOT

a	\bar{a}
0	1
1	0




$NOT\ a = \bar{a}$

CMOS inverter operation

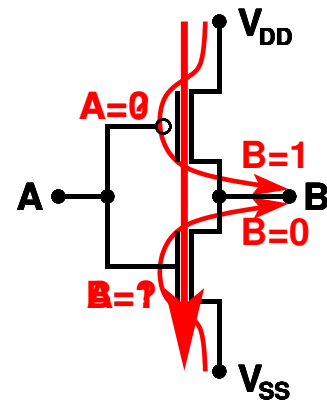


NAND operation

 


NAND gate

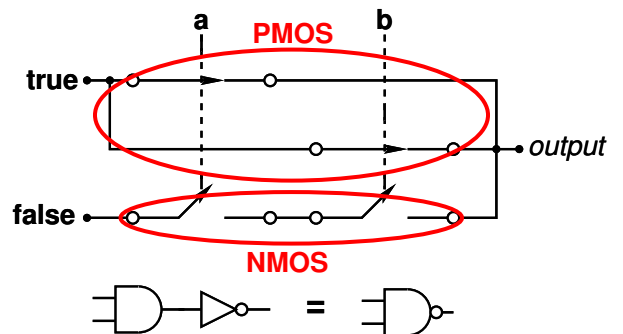
- Therefore, *NAND* and *NOR* gates are used in CMOS design instead of *AND* and *OR* gates



NAND layout

 

NOR operation

 


CMOS transmission gates (switches)

- NMOS is good at transmitting 0s
 - Bad at transmitting 1s
- PMOS is good at transmitting 1s
 - Bad at transmitting 0s
- To build a switch, use both: CMOS

21

Robert Dick

Digital Integrated Circuits

 


CMOS transmission gate (TG)

22

Robert Dick

Digital Integrated Circuits

Other TG diagram

 

23

Robert Dick

Digital Integrated Circuits

Logic gates vs. TGs

- What can each be used to implement?
- How to decide which to use?

24

Robert Dick

Digital Integrated Circuits

Upcoming topics

- Diodes.
- Transistor static behavior.
- Transistor dynamic behavior.

25

Robert Dick

Digital Integrated Circuits

Homework assignment and announcement

- 12 September: Read Section 3.3.2 in J. Rabaey, A. Chandrakasan, and B. Nikolic. *Digital Integrated Circuits: A Design Perspective*. Prentice-Hall, second edition, 2003.
- 17 September: Laboratory assignment one.

27

Robert Dick

Digital Integrated Circuits